

O m3dulo de interface com o mecanismo da porta (Serial Door Controller, SDC) implementa a rece3o em s3rie da informa3o enviada pelo m3dulo de controlo, entregando-a posteriormente ao mecanismo da porta, conforme representado na Figura 1.

 


Figura 1 – Diagrama de blocos do m3dulo *Serial Door Controller*

1 Serial Receiver

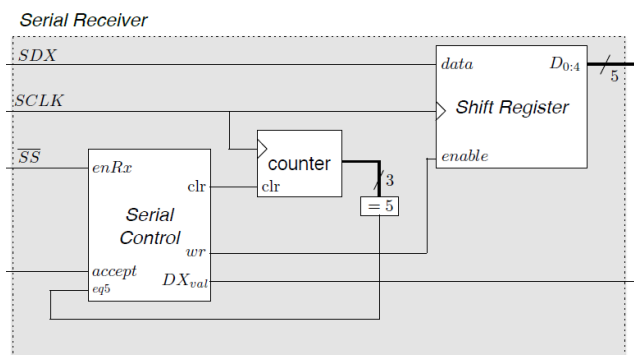


Figura 2 – Diagrama de Blocos do bloco *Serial Receiver*

O bloco Serial Receiver 3 utilizado tanto no m3dulo Serial LCD Controller como no m3dulo Serial Door Controller, desta forma foi poss3vel reutilizar o bloco Serial Receiver nos dois m3dulos.

O SDC recebe em s3rie uma mensagem constitu3da por cinco bits de informa3o. A comunica3o com o SDC realiza-se, tendo como primeiro bit de informa3o, o bit *OpenClose* (OC) que indica se o comando 3 para abrir ou fechar a porta. Os restantes bits cont3m a informa3o da velocidade de abertura ou fecho. O SDC indica que est3 dispon3vel para a rece3o de uma nova trama ap3s ter processado a trama anterior, colocando o *busy* no n3vel l3gico “0”.

O bloco *Serial Control* foi implementado pela m3quina de estados representada em *ASM-chart* na Figura 3.

Inicialmente o Serial Control encontra-se estado 00 o sinal Clr est3 ativo de forma que o counter permanea inativo at3 que o valor l3gico do sinal SS seja 0 indicando que o envio de dados ir3 com3ear. Enquanto permanece no estado 01 o sinal WR fica ativo e permanece ativo at3 que sejam contados 5 bits na transfer3ncia de dados. Quando o n3mero de bits recebidos atinge o valor 5 ocorre uma passagem para

o estado 10, e permanece neste at3 que o sinal SS esteja com o valor l3gico 1 indicando que o envio de dados terminou. Quando o envio de dados termina, ocorre uma mudana para o estado 11 onde aguarda at3 que o valor l3gico do sinal *accept* seja 1, indicando a trama foi processada e *accept* seja 1, indicando a trama foi processada, ativando os sinais *DXval* e *busy*.

A descri3o hardware do bloco *Serial Receiver* em VHDL encontra-se no Anexo A.

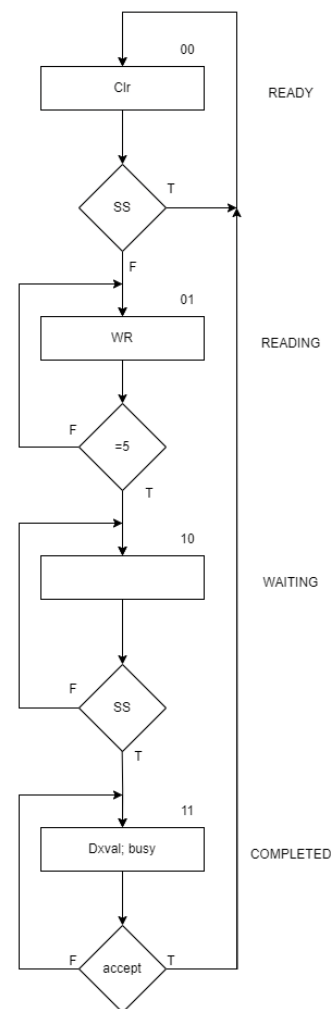


Figura 3 – M3quina de estados do bloco *Serial Control*

3 Door Controller

O bloco Door Controller, ap3s este ter recebido uma trama v3lida recebida pelo Serial Receiver, dever3 proceder 3 atua3o do comando recebido no mecanismo da porta. Se o comando recebido for de abertura, o Door Controller dever3 colocar o sinal *OnOff* o sinal *OpenClose* no valor l3gico ‘1’, at3 o sensor de porta aberta (*FCopen*) ficar ativo. No

entanto, se o comando for de fecho, o Door Controller dever ativar o sinal $On\overline{ff}$ e colocar o sinal $Open\overline{Close}$ no valor lgico ‘0’, at o sensor de porta fechada ($FC\overline{close}$) ficar ativo. Se durante o fecho for detetada uma pessoa na zonada porta, atravs do sensor de presena ($Pdetect$), o sistema dever interromper o fecho reabrindo a porta. Aps a interrupo do fecho da porta, o bloco Door Controller dever permitir de forma automtica, ou seja, sem necessidade de envio de uma nova trama, o encerramento da porta e o finalizar do comando de fecho .Aps concluir qualquer um dos comandos, o Door Controller sinaliza o Serial Receiver que est pronto para processar uma nova trama atravs da ativao do sinal done.

O bloco *Door Controller* foi implementado pela mquina de estados representada em *ASM-chart* na Figura 4.

A descrio hardware do bloco *Door Controller* em VHDL encontra-se no Anexo B.

Inicialmente o bloco Door Controller encontra-se no estado 000, a aguardar que o nvel lgico do sinal Dval seja ‘1’ indicando uma trama vlida. Quando recebe a indicao de uma trama vlida, verifica o sinal OC de forma a apurar se o comando  para abrir ou fechar a porta. Se o comando  de  para abrir a porta, ocorre uma mudana para o estado 001, onde permanece com os sinais $On\overline{ff}$ (ativando o mecanismo da porta) e $Open\overline{Close}$ ativos at que esta esteja completamente aberta , aguardando que o sinal Sopen tenha valor lgico ‘1’. De seguida verifica se a instruo  de fecho de forma a concluir a mesma, se a instruo  de abrir a porta, ocorre a passagem para o estado 100 em que o sinal done  ativado onde aguarda que o sinal Dval tenha valor lgico ‘0’. Se pelo contrrio a instruo  de fechar a porta, a mquina de estados passa do estado 000 para o estado 010 onde verifica atravs do sinal $Psensor$ se foi detetada alguma pessoa na zona da porta. Se no for detetada uma pessoa na zona da porta, passa para o estado 011 onde ativa o sinal $On\overline{ff}$, de forma a ativar o mecanismo da porta e com o sinal $Open\overline{Close}$ com valor lgico a ‘0’ indicando que  para fechar a porta, e permanece neste estado at que a porta esteja fechada, ativando o sinal $Scloes$. Se for detetada uma pessoa durante o fecho da porta ocorre uma passagem para o estado 001 de forma a abrir a porta. Depois de fechar a porta ocorre a passagem para o estado 100 ativando o sinal done informando que terminou de executar a instruo e aguarda que o sinal Dval tenha valor lgico ‘0’

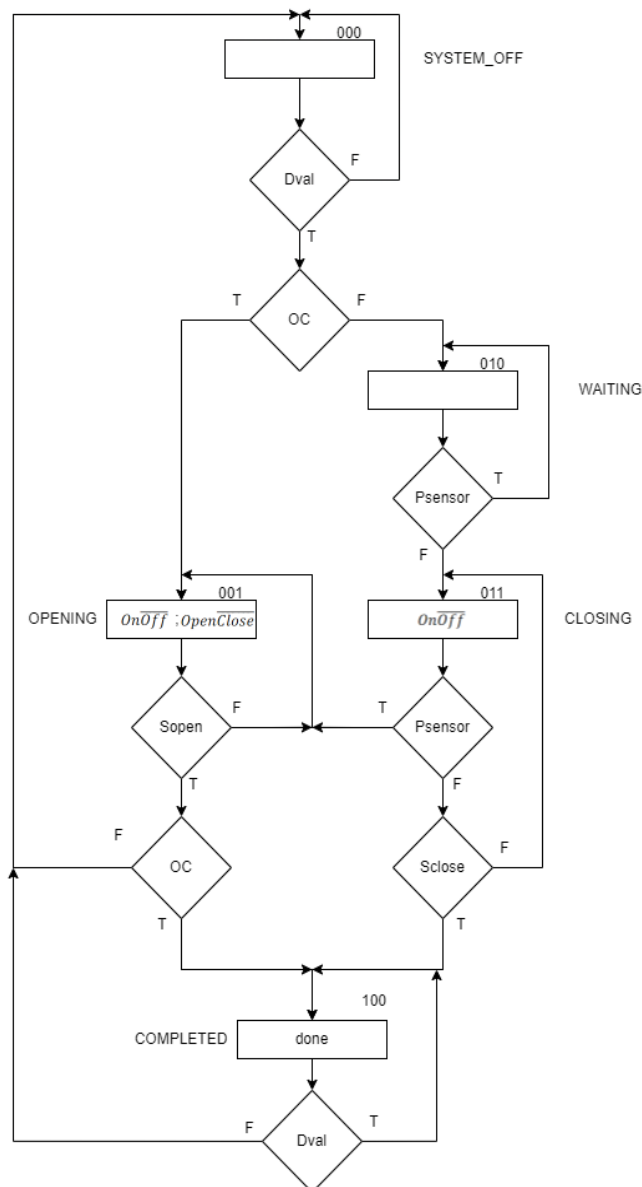


Figura 4 – Mquina de estados do bloco *Door Controller*

Com base nas descrio dos blocos *Serial Receiver* e *Door Controller* implementou-se o mdulo *Serial Door Controller* de acordo com o esquema eltrico representado no Anexo C.

4 Interface com o Control

Implementou-se o m3dulo *Control* em *software*, recorrendo a linguagem *Kotlin* e seguindo a arquitetura l3gica apresentada na Figura 8.

 


Figura 5 – Diagrama l3gico do m3dulo *Control* de interface com o m3dulo *Serial Door Controller*

HAL, *Serial Emitter* e *LCD* desenvolvidos s3o descritos nas s3c3es 4.1, 4.2 e 4.3, e o c3digo fonte desenvolvido nos Anexos C e D, respetivamente.

4.1 HAL

A classe *HAL* 3 respons3vel por comunicar com o bloco *UsbPort*, fazendo a leitura e a escrita no bloco *UsbPort*.

De forma a evitar efetuar a leitura do bloco *UsbPort* repetidamente foi criada uma vari3vel global (*written*) dentro da classe para guardar o 3ltimo valor escrito.

Nesta classe temos a fun3o *init* que inicia a classe, a fun3o *isBit()* que retorna *true* se o bit passado na m3scara tiver o valor l3gico 1. A fun3o *readBits()* efetua uma leitura tal como a fun3o *isBit()* mas para um conjunto de bits.

A fun3o *writeBits()* escreve um valor num conjunto de bits,

a fun3o *setBits()* escreve nos bits da m3scara o valor l3gico 1. E a fun3o *clrBits()* coloca o valor l3gico 0 no bit indicado na m3scara.

4.2 Serial Emitter

A classe *Serial Emitter* 3 respons3vel pelo envio de tramas para os diferentes m3dulos *Serial Receiver*.

De forma a distinguir os diferentes sinais necess3rios para a execu3o do m3dulo *SLCDC*, estes foram mapeados com o objetivo de serem obtidos e identificados no *outputPort* do m3dulo *UsbPort*.

A fun3o *send()* implementada nesta fase 3 respons3vel por criar a situa3o de envio de uma trama para os m3dulos *SLCDC* e *SDC*.

4.3 Door Mechanism

A classe *Door Mechanism* 3 respons3vel por controlar o estado do mecanismo de fecho e de abertura da porta.

A fun3o *open()* envia um comando para abrir a porta, com a velocidade passada com par3metro.

A fun3o *close()* envia um comando para fechar a porta, com a velocidade passada com par3metro.

A fun3o *finished()* verifica se o comando anterior est3 concluído.

5 Conclus3es

O m3dulo *SDC* tem como objetivo entregar a informa3o que lhe chega por parte do *Control* em forma de uma trama de 5 bits ao *Door Mechanism*. Para isso, implement3mos o *Serial Receiver*, respons3vel pela rece3o dos dados enviados pelo microcontrolador, e o bloco *Door Controller* que tem a fun3o de entregar os dados recebidos ao *Door Mechanism* ap3s a trama ser validada. O m3dulo *Serial Receiver* foi testado no simulador e posteriormente na placa, apresentando um funcionamento correto. O m3dulo *Door Controller* foi testado no simulador. O m3dulo *SDC_USBPORT* foi testado na placa onde apresentou um funcionamento correto.

A. Descrição VHDL do bloco *Serial Receiver*

Serial Control

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity SerialControl is
5  port( SS,clk,accept,eq5,reset : IN STD_LOGIC;
6        clr, wr, DXval, busy : OUT STD_LOGIC
7  );
8  end SerialControl;
9
10 architecture arq_SerialControl of SerialControl is
11
12 type STATE_TYPE is (READY, READING, WAITING,COMPLETED);
13
14 signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
15
16 begin
17
18     -- Registo Current State
19
20     CURRENT_STATE <= READY when (reset = '1') else NEXT_STATE when rising_edge(clk);
21
22     -- Máquina de Estados
23
24     GenerateNextState:
25     process (CURRENT_STATE, SS, eq5, accept)
26     begin
27         case CURRENT_STATE is
28             when READY => if(SS = '0') then
29                             NEXT_STATE <= READING;
30                         else
31                             NEXT_STATE <= READY;
32                         end if;
33
34             when READING => if(eq5 = '0') then
35                             NEXT_STATE <= READING;
36                         else
37                             NEXT_STATE <= WAITING;
38                         end if;
39
40             when WAITING => if(SS = '1') then
41                             NEXT_STATE <= COMPLETED;
42                         else
43                             NEXT_STATE <= WAITING;
44                         end if;
45
46             when COMPLETED => if(accept <= '0') then
47                             NEXT_STATE <= COMPLETED;
48                         else
49                             NEXT_STATE <= READY;
50                         end if;
51
52         end case;
53     end process;
54
55     -- Outputs
56     clr <= '1' when (CURRENT_STATE = READY) else '0';
57     wr <= '1' when (CURRENT_STATE = READING) else '0';
58     DXval <= '1' when (CURRENT_STATE = COMPLETED) else '0';
59     busy <= '1' when (CURRENT_STATE = COMPLETED) else '0';
60
61 end arq_SerialControl;

```

Counter

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY COUNTER_3 IS
5      PORT(
6          CLK : in std_logic;
7          E : in std_logic;
8          CLR: in std_logic;
9          R : out std_logic_vector (2 downto 0) :=(others => '0')
10     );
11 END COUNTER_3;
12
13
14 ARCHITECTURE arq_COUNTER OF COUNTER_3 IS
15
16     COMPONENT REGISTOR_RB IS
17     PORT( R : in std_logic_vector(2 downto 0);
18           CLR : in std_logic;
19           CL : in std_logic;
20           E : in std_logic;
21           TC : out std_logic;
22           F : out std_logic_vector (2 downto 0)
23     );
24     END COMPONENT;
25
26
27
28     COMPONENT SOMADOR3
29     PORT( A : in std_logic_vector(2 downto 0):=(others => '0');
30           B : in std_logic_vector(2 downto 0);
31           CI : in std_logic;
32           R : out std_logic_vector (2 downto 0):=(others => '0')
33     );
34     END COMPONENT;
35
36     SIGNAL SR: std_logic_vector(2 downto 0):=(others => '0');
37     SIGNAL RS: std_logic_vector(2 downto 0):=(others => '0');
38
39
40
41 BEGIN
42
43
44     USOMADOR : SOMADOR3 port map (
45         A => RS,
46         B(0) => '1',
47         B(1) => '0',
48         B(2) => '0',
49         CI => '0',
50         R => SR
51     );
52
53
54     UREGISTOR : REGISTOR_RB port map (
55         R => SR,
56         CL => CLK,
57         E => E,
58         F => RS,
59         CLR => CLR
60     );
61
62     R <= RS;
63 END arq_COUNTER;

```

Shift Register

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity ShiftRegister_SR is
5  port( Sin, CLK, enable, RST: in STD_LOGIC;
6        D : OUT STD_LOGIC_VECTOR(4 downto 0)
7  );
8  end ShiftRegister_SR;
9
10 architecture arq_ShiftRegister_SR of ShiftRegister_SR is
11
12 component ffd
13
14 port(CLK : in std_logic;
15       RESET : in STD_LOGIC;
16       SET : in std_logic;
17       D : IN STD_LOGIC;
18       EN : IN STD_LOGIC;
19       Q : out std_logic
20 );
21 end component;
22
23 signal DSignal: STD_LOGIC_VECTOR(4 downto 0);
24
25 begin
26
27 D(0)<=DSignal(4);
28 D(1)<=DSignal(3);
29 D(2)<=DSignal(2);
30 D(3)<=DSignal(1);
31 D(4)<=DSignal(0);
32
33 Uffd0 : ffd port map (
34     CLK => CLK,
35     RESET => RST,
36     SET => '0',
37     D => Sin,
38     EN => enable,
39     Q => DSignal(0)
40 );
41
42 Uffd1 : ffd port map (
43     CLK => CLK,
44     RESET => RST,
45     SET => '0',
46     D => DSignal(0),
47     EN => enable,
48     Q => DSignal(1)
49 );
50
51 Uffd2 : ffd port map (
52     CLK => CLK,
53     RESET => RST,
54     SET => '0',
55     D => DSignal(1),
56     EN => enable,
57     Q => DSignal(2)
58 );
59
60 Uffd3 : ffd port map (
61     CLK => CLK,
62     RESET => RST,
63     SET => '0',
64     D => DSignal(2),
65     EN => enable,
66     Q => DSignal(3)
67 );
68
69 Uffd4 : ffd port map (
70     CLK => CLK,
71     RESET => RST,
72     SET => '0',
73     D => DSignal(3),
74     EN => enable,
75     Q => DSignal(4)

```

```

76 );
77
78
79 end arq_ShiftRegister_SR;

```

Serial Receiver

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity SerialReceiver is
5  port(
6      SDX, SCLK, SS, accept, MCLK, reset : in std_logic;
7      DXval, busy : out std_logic;
8      data : out std_logic_vector (4 downto 0)
9  );
10
11  end SerialReceiver;
12
13  architecture arq_SerialReceiver OF SerialReceiver IS
14
15
16  component COUNTER_3
17  PORT(
18      CLK : in std_logic;
19      E: in std_logic;
20      CLR: in std_logic;
21      R : out std_logic_vector (2 downto 0) :=(others => '0')
22  );
23  end component;
24
25
26  component ShiftRegister_SR
27  port( Sin, CLK, enable, RST: in STD_LOGIC;
28      D : OUT STD_LOGIC_VECTOR(4 downto 0)
29  );
30  end component;
31
32
33  component equalTo5
34  port( D : IN STD_LOGIC_VECTOR(2 downto 0);
35      F : OUT STD_LOGIC
36  );
37  end component;
38
39
40  component SerialControl
41  port( SS,clk,accept,eq5,reset : IN STD_LOGIC;
42      clr, wr, DXval, busy : OUT STD_LOGIC
43  );
44  end component;
45
46
47
48  signal wrSignal, clrSignal, eq5Signal, Clk_signal : STD_LOGIC;
49  signal counterSignal : std_logic_vector(2 downto 0);
50
51  begin
52
53
54  uSerialControl : SerialControl port map(
55      SS => SS,
56      clk => MCLK,
57      accept => accept,
58      wr => wrSignal,
59      clr => clrSignal,
60      DXval => DXval,
61      reset => reset,
62      eq5 => eq5Signal,
63      busy => busy
64  );
65

```



```
66  uShiftRegister : ShiftRegister_SR port map(  
67      Sin => SDX,  
68      CLK => SCLK,  
69      enable => wrSignal,  
70      RST => reset,  
71      D => data  
72  );  
73  
74  uCOUNTER_3 : COUNTER_3 port map(  
75      CLK => SCLK,  
76      E => wrSignal,  
77      CLR => clrSignal,  
78      R => counterSignal  
79  );  
80  
81  uequalTo5 : equalTo5 port map (  
82      D=>counterSignal,  
83      F=>eq5Signal  
84  );  
85  
86  end arq_SerialReceiver;
```


B. Descrição VHDL do bloco *Door Controller*

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity DoorController is
5  port( Dval,clk,reset, Sclose, Sopen, Psensor : IN STD_LOGIC;
6        OnOff, done, OpenClose : OUT STD_LOGIC;
7        Din : IN STD_LOGIC_VECTOR(4 downto 0);
8        Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
9  );
10 end DoorController;
11
12 architecture behavioral of DoorController is
13
14
15  type STATE_TYPE is (SYSTEM_OFF, WAITING, OPENING, CLOSING, COMPLETED);
16
17  signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
18
19  begin
20
21  --    Registo Current State
22
23  CURRENT_STATE <= SYSTEM_OFF when (reset = '1') else NEXT_STATE when rising_edge(clk);
24
25  --    Máquina de Estados
26
27  GenerateNextState:
28  process (CURRENT_STATE, Dval, Sclose, Sopen, Psensor, Din)
29  begin
30      case CURRENT_STATE is
31          when SYSTEM_OFF => if(Dval = '1' and Din(0) = '1') then
32                               NEXT_STATE <= OPENING;
33                           elsif(Dval = '1' and Din(0) = '0') then
34                               NEXT_STATE <= WAITING;
35                           else
36                               NEXT_STATE <= SYSTEM_OFF;
37                           end if;
38
39          when WAITING => if(Psensor = '0') then
40                               NEXT_STATE <= CLOSING;
41                           else
42                               NEXT_STATE <= WAITING;
43                           end if;
44          when OPENING => if(Sopen = '0') then
45                               NEXT_STATE <= OPENING;
46                           elsif(Sopen = '1' and Din(0) = '1') then
47                               NEXT_STATE <= COMPLETED;
48                           elsif(Sopen = '1' and Din(0) = '0') then
49                               NEXT_STATE <= SYSTEM_OFF;
50                           end if;
51          when CLOSING => if(Psensor = '1') then
52                               NEXT_STATE <= OPENING;
53                           elsif(Sclose = '1') then
54                               NEXT_STATE <= COMPLETED;
55                           else
56                               NEXT_STATE <= CLOSING;
57                           end if;
58          when COMPLETED => if(Dval = '0') then
59                               NEXT_STATE <= SYSTEM_OFF;
60                           else
61                               NEXT_STATE <= COMPLETED;
62                           end if;
63      end case;
64  end process;
65
66  end case;
67
68  end process;
69

```

```
69 end process;
70
71 -- Outputs
72 OnOff <= '1' when (CURRENT_STATE = OPENING OR CURRENT_STATE = CLOSING) else '0';
73 OpenClose <= '1' when (CURRENT_STATE = OPENING) else '0';
74 done <= '1' when (CURRENT_STATE = COMPLETED) else '0';
75 Dout <= Din;
76
77 end behavioral;
```

C. Descrição VHDL do bloco SDC

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY SDC IS
5      PORT( MCLK,reset : IN STD_LOGIC;
6            NOT_SS, SCLK, SDX, Sclose, Sopen, Psensor: IN STD_LOGIC; --software
7            OnOff, busy : OUT STD_LOGIC;
8            Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
9      );
10 END SDC;
11
12
13 ARCHITECTURE arq_SDC OF SDC IS
14
15     component COUNTER
16     PORT( CLK : in std_logic;
17           E : in std_logic;
18           clr: in std_logic;
19           R : out std_logic_vector (3 downto 0)
20         );
21     end component;
22
23
24
25
26
27     COMPONENT SerialReceiver
28     port(
29         SDX, SCLK, SS, accept, MCLK, reset : in std_logic;
30         DXval, busy : out std_logic;
31         data : out std_logic_vector (4 downto 0)
32     );
33     END COMPONENT;
34
35     COMPONENT DoorController
36     port( Dval,clk,reset, Sclose, Sopen, Psensor : IN STD_LOGIC;
37           OnOff, done, OpenClose : OUT STD_LOGIC;
38           Din : IN STD_LOGIC_VECTOR(4 downto 0);
39           Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
40     );
41     END COMPONENT;
42
43     COMPONENT CLKDIV is
44     generic(div: natural := 50000000);
45     port ( clk_in: in std_logic;
46           clk_out: out std_logic);
47     END COMPONENT;
48
49     signal DXvalSignal, SCLKSignal, MCLKDivSignal, acceptDoneSignal: STD_LOGIC;
50     signal DataSignal, DoutSignal : STD_LOGIC_VECTOR (4 downto 0);
51     signal counterSignal : STD_LOGIC_VECTOR (3 downto 0);
52
53     begin
54
55
56     --uCLKDIV : CLKDIV generic map(2) port map(
57         -- clk_in => MCLK,
58         -- clk_out => MCLKDivSignal
59     --);
60

```

```
61  uSerialReceiver: SerialReceiver PORT MAP (  
62      SDX      => SDX,  
63      SCLK     => SCLK,  
64      SS       => NOT_SS,  
65      accept   => acceptDoneSignal,  
66      MCLK     => MCLK,--MCLKDivSignal,  
67      reset    => reset,  
68      DXval    => DXvalSignal,  
69      data     => DataSignal,  
70      busy     => busy  
71  );  
72  
73  uDoorController: DoorController PORT MAP (  
74      Dval     => DXvalSignal,  
75      clk      => MCLK,--MCLKDivSignal,  
76      reset    => reset,  
77      done     => acceptDoneSignal,  
78      Din      => DataSignal,  
79      Dout     => Dout,  
80      Sclose   => Sclose,  
81      Sopen    => Sopen,  
82      Psensor  => Psensor  
83  );  
84  
85  end arq_SDC;  
86  
87
```

D. Descrição VHDL do bloco *SDC_USBPORT*

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY SDC_USBPORT IS
5      PORT(
6          MCLK,reset, Pswitch, Sopenin, Sclosein : IN STD_LOGIC;
7          Dout : out std_logic_vector(4 downto 0);
8          onOff, OpenClose, Psensor : out std_logic;
9          HEX0      : out std_logic_vector(7 downto 0);
10         HEX1      : out std_logic_vector(7 downto 0);
11         HEX2      : out std_logic_vector(7 downto 0);
12         HEX3      : out std_logic_vector(7 downto 0);
13         HEX4      : out std_logic_vector(7 downto 0);
14         HEX5      : out std_logic_vector(7 downto 0)
15     );
16 END SDC_USBPORT;
17
18
19
20
21 ARCHITECTURE arq_SDC_USBPORT OF SDC_USBPORT IS
22
23 COMPONENT UsbPort
24     PORT
25     (
26         inputPort: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
27         outputPort : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
28     );
29 END COMPONENT;
30
31 COMPONENT SDC
32     PORT(
33         MCLK,reset : IN STD_LOGIC;
34         NOT_SS, SCLK, SDX, Sclose, Sopen, Psensor: IN STD_LOGIC; --software
35         OnOff, busy, OpenClose : OUT STD_LOGIC;
36         Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
37     );
38 END COMPONENT;
39
40 COMPONENT door_mecanism IS
41     PORT( MCLK
42         : in std_logic;
43         RST
44         : in std_logic;
45         onOff
46         : in std_logic;
47         openClose
48         : in std_logic;
49         v
50         : in std_logic_vector(3 downto 0);
51         Pswitch
52         : in std_logic;
53         Sopen
54         : out std_logic;
55         Sclose
56         : out std_logic;
57         Pdetector
58         : out std_logic;
59         HEX0
60         : out std_logic_vector(7 downto 0);
61         HEX1
62         : out std_logic_vector(7 downto 0);
63         HEX2
64         : out std_logic_vector(7 downto 0);
65         HEX3
66         : out std_logic_vector(7 downto 0);
67         HEX4
68         : out std_logic_vector(7 downto 0);
69         HEX5
70         : out std_logic_vector(7 downto 0)
71     );
72 END COMPONENT;
73
74
75
76
77 signal UsbPortInputSignal, UsbPortOutputSignal : STD_LOGIC_VECTOR (7 downto 0);
78 signal ScloseSignal, SopenSignal, PsensorSignal, OnOffSignal: STD_LOGIC;
79 signal DoutSignal :STD_LOGIC_VECTOR(4 downto 0);
80
81 begin
82
83
84
85
86
87
88
89
90
91
92
93
94
95
96
97
98
99

```

```

69  uUsbPort: UsbPort PORT MAP(
70      inputPort  => UsbPortInputSignal,
71      outputPort => UsbPortOutputSignal
72  );
73
74
75  uSDC: SDC PORT MAP(
76      MCLK      => MCLK,
77      reset     => reset,
78
79      NOT_SS    => UsbPortOutputSignal(2), --0x04
80      SCLK      => UsbPortOutputSignal(1), --0x02
81      SDX       => UsbPortOutputSignal(0), --0x01
82      Sclose    => Sclosein,
83      Sopen     => Sopenin,
84      Psensor   => Pswitch,
85      OnOff     => OnOffSignal,
86      OpenClose => OpenClose,
87      busy      => UsbPortInputSignal(7), --0x80
88      Dout      => DoutSignal
89  );
90
91
92  --udoor_mecanism: door_mecanism PORT MAP (
93      -- MCLK      => MCLK,
94      -- RST       => reset,
95      --onOff      => OnOffSignal,
96      --openClose => DoutSignal(0), --OC
97      --v          => DoutSignal (4 downto 1),
98      --Pswitch    => Pswitch,
99      --Sopen      => SopenSignal,
100     -- Sclose     => ScloseSignal,
101     -- Pdetector  => PsensorSignal,
102     --HEX0        => HEX0,
103     ---HEX1       => HEX1,
104     -- HEX2       => HEX2,
105     --HEX3        => HEX3,
106     --HEX4        => HEX4,
107     --HEX5        => HEX5
108     --);
109
110     Dout <= DoutSignal;
111     onOff <= OnOffSignal;
112     --Sopen <= SopenSignal;
113     --Sclose <= ScloseSignal;
114     Psensor <= Pswitch;
115
116 end arq_SDC_USBPORT;

```

E. Atribuio de pinos do mdulo *SDC_USBPORT*

CLOCK

#

set_location_assignment PIN_P11 -to MCLK

#

SW

#

set_location_assignment PIN_C10 -to reset

set_location_assignment PIN_C11 -to Pswitch

set_location_assignment PIN_D12 -to Sopenin

set_location_assignment PIN_C12 -to Sclosein

#LED

set_location_assignment PIN_A8 -to Dout[0]

set_location_assignment PIN_A9 -to Dout[1]

set_location_assignment PIN_A10 -to Dout[2]

set_location_assignment PIN_B10 -to Dout[3]

set_location_assignment PIN_D13 -to Dout[4]

set_location_assignment PIN_C13 -to onOff

#set_location_assignment PIN_E14 -to Sopen

#set_location_assignment PIN_D14 -to Sclose

set_location_assignment PIN_A11 -to Psensor

set_location_assignment PIN_B11 -to OpenClose

#

HEX0

#

set_location_assignment PIN_C14 -to HEX0[0]

set_location_assignment PIN_E15 -to HEX0[1]

set_location_assignment PIN_C15 -to HEX0[2]

set_location_assignment PIN_C16 -to HEX0[3]

set_location_assignment PIN_E16 -to HEX0[4]

set_location_assignment PIN_D17 -to HEX0[5]

set_location_assignment PIN_C17 -to HEX0[6]

set_location_assignment PIN_D15 -to HEX0[7]

#

HEX1

#

set_location_assignment PIN_C18 -to HEX1[0]

set_location_assignment PIN_D18 -to HEX1[1]

set_location_assignment PIN_E18 -to HEX1[2]

set_location_assignment PIN_B16 -to HEX1[3]

set_location_assignment PIN_A17 -to HEX1[4]

set_location_assignment PIN_A18 -to HEX1[5]

set_location_assignment PIN_B17 -to HEX1[6]

set_location_assignment PIN_A16 -to HEX1[7]

#=====

HEX2

#=====

set_location_assignment PIN_B20 -to HEX2[0]

set_location_assignment PIN_A20 -to HEX2[1]

set_location_assignment PIN_B19 -to HEX2[2]

set_location_assignment PIN_A21 -to HEX2[3]

set_location_assignment PIN_B21 -to HEX2[4]

set_location_assignment PIN_C22 -to HEX2[5]

set_location_assignment PIN_B22 -to HEX2[6]

set_location_assignment PIN_A19 -to HEX2[7]

#=====

HEX3

#=====

set_location_assignment PIN_F21 -to HEX3[0]

set_location_assignment PIN_E22 -to HEX3[1]

set_location_assignment PIN_E21 -to HEX3[2]

set_location_assignment PIN_C19 -to HEX3[3]

set_location_assignment PIN_C20 -to HEX3[4]

et_location_assignment PIN_D19 -to HEX3[5]

set_location_assignment PIN_E17 -to HEX3[6]

set_location_assignment PIN_D22 -to HEX3[7]

#=====

HEX4

#=====

set_location_assignment PIN_F18 -to HEX4[0]

set_location_assignment PIN_E20 -to HEX4[1]

set_location_assignment PIN_E19 -to HEX4[2]

set_location_assignment PIN_J18 -to HEX4[3]

set_location_assignment PIN_H19 -to HEX4[4]

set_location_assignment PIN_F19 -to HEX4[5]

set_location_assignment PIN_F20 -to HEX4[6]

set_location_assignment PIN_F17 -to HEX4[7]

#=====

HEX5

#=====

set_location_assignment PIN_J20 -to HEX5[0]

set_location_assignment PIN_K20 -to HEX5[1]

set_location_assignment PIN_L18 -to HEX5[2]

set_location_assignment PIN_N18 -to HEX5[3]

set_location_assignment PIN_M20 -to HEX5[4]

set_location_assignment PIN_N19 -to HEX5[5]

set_location_assignment PIN_N20 -to HEX5[6]

set_location_assignment PIN_L19 -to HEX5[7]

#=====

End of pin and io_standard assignments

#=====

F. C3digo Kotlin - HAL

```
object HAL {
    var written = 0b0000_0000
    private var ACTIVE = false
    fun init() { // Inicia a classe
        if(!ACTIVE) {
            UsbPort.write(written)
            ACTIVE=true
        }
    }

    // Retorna true se o bit tiver o valor l3gico '1'
    fun isBit(mask: Int): Boolean = (mask and UsbPort.read()) != 0

    // Retorna os valores dos bits representados por mask presentes no UsbPort
    fun readBits(mask: Int): Int = mask and UsbPort.read()

    // Escreve nos bits representados por mask o valor de value
    /**
     * value -> 0000_1001.
     * mask -> 0000_1111.
     * lastWritten -> 1111_0111.
     * new lastWritten -> 1111_1001.
     * 1º: (value and mask) -> 0000_1001 sets the bits in value to be written to the ones in the
     mask.
     * 2º: (lastWritten and mask.inv()) -> 1111_0000 sets the bits in lastWritten that are not
     in the mask,this operation
     *     sets to 0 all the bits in lastWritten that are not in the mask, preparing it to
     receive the updated value.
     * 3º: (value and mask) or (lastWritten and mask.inv()) -> 0000_1001 or 1111_0000 ->
     1111_1001 sets the bits in
     *     lastWritten that are in the mask to the corresponding bits in value and keeps the
     bits that are not in the mask unchanged.
     */

    fun writeBits(mask: Int, value: Int) {
        written = (value and mask) or (written and mask.inv())
        UsbPort.write(written)
    }

    // Coloca os bits representados por mask no valor l3gico '1'
    fun setBits(mask: Int) {
        written = (written or mask)
        UsbPort.write(written)
    }

    // Coloca os bits representados por mask no valor l3gico '0'
    fun clrBits(mask: Int) {
        written = written and mask.inv()
        UsbPort.write(written)
    }
}
```

G. C3digo Kotlin – Serial Emitter

```
/**
 * Mapeamento
 *      n      7      6      5      4      3      2      1      0
 * inputPort :BSY  0      0      0      0      0      0      0      0      //inputPort(n)
 * outPort   : 0      0      0      0      LCD DOOR SCLK SDX //outputPort(n)
 *
 *                      SS      SS
 * D[0:4] :    -      -      -      D(3) D(2) D(1) D(0) RS
 */

object SerialEmitter {    // Envia tramas para os diferentes m3dulos Serial Receiver
    enum class Destination {LCD, DOOR}
    private const val MASK_BUSY = 0x80
    private const val MASK_NOT_SS_LCD = 0x08
    private const val MASK_NOT_SS_DOOR = 0x04
    private const val MASK_SCLK = 0x02
    private const val MASK_SDx = 0x01
    private const val DATA_SIZE = 5

    // Inicia a classe
    fun init() {
        HAL.init()
        HAL.setBits(MASK_NOT_SS_LCD) // SS = 1
        HAL.setBits(MASK_NOT_SS_DOOR) // SS = 1
        HAL.clrBits(MASK_SCLK) // SCLK = 0
        HAL.clrBits(MASK_SDx) // SDx = 0
    }

    // Envia uma trama para o SerialReceiver identificado o destino em addr e os bits de dados em 'data'.
    fun send(addr: Destination, value: Int) {
        var data = value
        while (isBusy()) { }
        val address = if (addr == Destination.LCD) MASK_NOT_SS_LCD else MASK_NOT_SS_DOOR
        for (i in 0 until DATA_SIZE) {
            HAL.clrBits(MASK_SCLK) // SCLK = 0
            HAL.clrBits(address) // SS = 0
            HAL.writeBits(0x01, 0x01 and data) // SDx = data[0]
            data = data shr 1 // data = data >> 1 to send bit a bit
            HAL.setBits(MASK_SCLK) // SCLK = 1
        }
        HAL.clrBits(0x01) // SDx = 0
        HAL.clrBits(MASK_SCLK) // SCLK = 0
        HAL.setBits(address) // SS = 1
    }

    // Retorna true se o canal s3erie estiver ocupado
    fun isBusy(): Boolean = HAL.isBit(MASK_BUSY)
}
```

H. Código Kotlin – Door Mechanism

```
/*
 * Enviar pelo SerialEmmitter tal como no LCD
 * Dados:      D4  D3  D2  D1  D0
 *             V3  V2  V1  V0  OC
 *
 * OC -> 0 Fechar | 1 Abrir
 * V3..0 -> Velocidade
 * */

object DoorMechanism {    // Controla o estado do mecanismo de abertura da porta.

    // Inicia a classe, estabelecendoos valores iniciais.
    fun init() {
        SerialEmitter.init()
    }
    // Envia comando para abrir a porta, com o parâmetro de velocidade
    fun open(velocity: Int) {
        SerialEmitter.send(SerialEmitter.Destination.DOOR, (velocity shl 1) or 1)
//D4..1 -> Velocidade | D0 -> OC -> 1 Abrir
    }
    // Envia comando para fechar a porta, com o parâmetro de velocidade
    fun close(velocity: Int) {
        SerialEmitter.send(SerialEmitter.Destination.DOOR, (velocity shl 1 )or 0)
//D4..1 -> Velocidade | D0 -> OC -> 0 Fechar
    }
    // Verifica se o comando anterior está concluído
    fun finished(): Boolean = !SerialEmitter.isBusy()
}
```