

O bloco *Serial Receiver* do *SLCDC*   constitu do por tr s blocos principais: *i*) um bloco de controlo; *ii*) um contador de bit srecebidos; e *iii*) um bloco conversor s rie paralelo, designados respetivamente por *Serial Control*, *Counter*, e *Shift*

 


Figura 1 – Diagrama de blocos do m dulo *Serial LCD Controller*

1 Serial Receiver

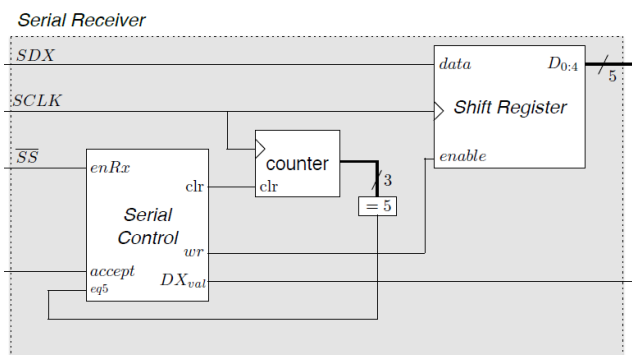


Figura 2 – Diagrama de Blocos do bloco *Serial Receiver*

O bloco *Serial Receiver*   utilizado tanto no m dulo *Serial LCD Controller* como no m dulo *Serial Door Controller*, desta forma foi poss vel reutilizar o bloco *Serial Receiver* nos dois m dulos.

O bloco *Serial Control* foi implementado pela m quina de estados representada em *ASM-chart* na Figura 3.

Inicialmente o *Serial Control* encontra-se estado 00 o sinal *Clr* est  ativo de forma que o counter permanea inativo at  que o valor l gico do sinal *SS* seja 0 indicando que o envio de dados ir  comear. Enquanto permanece no estado 01 o sinal *WR* fica ativo e permanece ativo at  que sejam contados 5 bits na transfer ncia de dados. Quando o n mero de bits recebidos atinge o valor 5 ocorre uma passagem para o estado 10, e permanece neste at  que o sinal *SS* esteja com o valor l gico 1 indicando que o envio de dados terminou. Quando o envio de dados termina, ocorre uma mudana para o estado 11 onde aguarda at  que o valor l gico do sinal *accept* seja 1, indicando a trama foi processada.

A descri o hardware do bloco *Serial Receiver* em VHDL encontra-se no Anexo A.

 


Figura 3 – M quina de estados do bloco *Serial Control*

3 Dispatcher

O bloco *Dispatcher* entrega a trama recebida pelo *Serial Receiver* ao *LCD* atrav s da ativa o do sinal *WrL*, ap s este ter recebido uma trama v lida, indicado pela ativa o do sinal *DX_val*.

O *LCD* processa as tramas recebidas de acordo com os comandos definidos pelo fabricante, n o sendo necess rio esperar pela sua execu o para libertar o canal de rece o s rie. Assim, o *Dispatcher* pode sinalizar ao *Serial Receiver* que a trama foi processada, ativando o sinal *done*.

O bloco *Dispatcher* foi implementado pela m quina de estados representada em *ASM-chart* na Figura 4.

A descri o hardware do bloco *Dispatcher* em VHDL encontra-se no Anexo B.

Inicialmente o bloco Dispatcher encontra-se no estado 00, a aguardar que o valor lógico do sinal Dval seja 1 indicando uma trama válida. Quando recebe a indicação de uma trama válida, ocorre uma mudança para o estado 01, onde permanece com o sinal WRL ativo (ativando o Enable do LCD) até que sejam atingidos 12 ciclos de relógio de forma a escrever no LCD (mínimo 230 ns).

Ao atingir os 12 ciclos de relógio ocorre a passagem para o estado 10 onde o sinal done é ativado e mantém-se no estado 10 até que o valor lógico do sinal Dval esteja desativado de modo a evitar múltiplas escritas, quando o sinal Dval estiver desativado regressa ao estado 00.

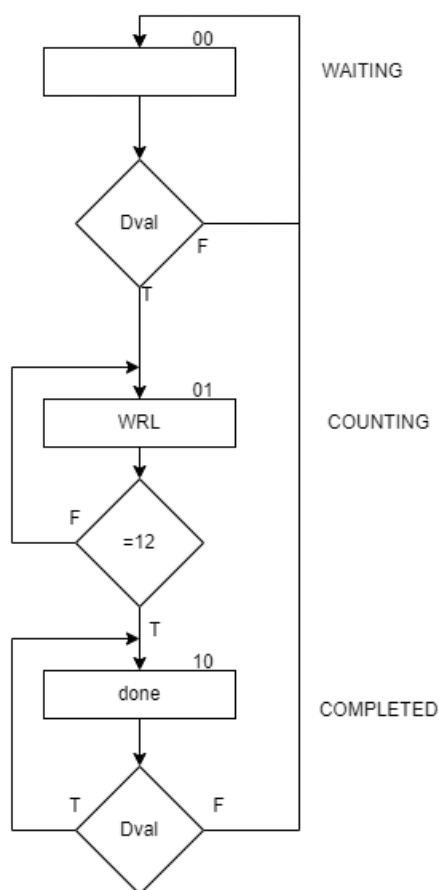


Figura 4 – Máquina de estados do bloco *Dispatcher*

Com base nas descriões dos blocos *Serial Receiver* e *Dispatcher* implementou-se o módulo *Serial LCD Controller* de acordo com o esquema elétrico representado no Anexo C.

4 Interface com o Control

Implementou-se o módulo *Control* em *software*, recorrendo a linguagem *Kotlin* e seguindo a arquitetura lógica apresentada na Figura 8.

 


Figura 5 – Diagrama lógico do módulo *Control* de interface com o módulo *Serial LCD Controller*

HAL, *Serial Emitter* e *LCD* desenvolvidos são descritos nas secões 4.1, 4.2 e 4.3, e o código fonte desenvolvido nos Anexos C e D, respetivamente.

4.1 HAL

A classe *HAL* é responsável por comunicar com o bloco *UsbPort*, fazendo a leitura e a escrita no bloco *UsbPort*.

De forma a evitar efetuar a leitura do bloco *UsbPort* repetidamente foi criada uma variável global (*written*) dentro da classe para guardar o último valor escrito.

Nesta classe temos a função *init* que inicia a classe, a função *isBit()* que retorna *true* se o bit passado na máscara tiver o valor lógico 1. A função *readBits()* efetua uma leitura tal como a função *isBit()* mas para um conjunto de bits.

A função *writeBits()* escreve um valor num conjunto de bits, a função *setBits()* escreve nos bits da máscara o valor lógico 1. E a função *clrBits()* coloca o valor lógico 0 no bit indicado na máscara.

4.2 Serial Emitter

A classe *Serial Emitter* é responsável pelo envio de tramas para os diferentes módulos *Serial Receiver*.

De forma a distinguir os diferentes sinais necessários para a execução do módulo *SLCDC*, estes foram mapeados com o objetivo de serem obtidos e identificados no *outputPort* do módulo *UsbPort*.

A função *send()* implementada nesta fase é responsável por criar a situação de envio de uma trama para os módulos *SLCDC* e *SDC*.

4.3 LCD

A classe LCD é responsável por escrever no LCD usando a interface a 4 bits.

A função `writeNibbleParalel()` escreve um nibble de comando ou dados no LCD em paralelo.

A função `writeNibbleSerial()` recorre à função `send()` do `SerialEmitter` para escrever um nibble de comando ou dados no LCD em série.

A função `writeNibble()` escreve um nibble de comandos ou dados no LCD.

A função `writeByte()` escreve um byte de comandos ou dados no LCD.

A função `writeCMD()` escreve um comando no LCD.

A função `writeDATA()` escreve dados no LCD.

A função `write(c:Char)` escreve um carácter na posição corrente

A função `write(c:String)` escreve uma string na posição corrente.

A função `cursor()` posiciona o cursor na posição desejada.

A função `clear()` limpa o ecrã e coloca o cursor em (0,0).

5 Conclusões

O módulo `SLCDC` tem como objetivo entregar a informação que lhe chega por parte do Control em forma de uma trama de 5 bits ao LCD. Para isso, implementámos o módulo `Serial Receiver`, responsável pela receção dos dados enviados pelo microcontrolador, e o bloco `Dispatcher` que tem a função de entregar os dados recebidos ao LCD após a trama ser validada. O módulo `Serial Receiver` foi testado no simulador e posteriormente na placa, apresentando um funcionamento correto. O módulo `Dispatcher` foi testado no simulador e mais tarde foi testado na placa, no módulo `SLCDC_USBPORT`, juntamente com o software, onde também observámos o correto funcionamento deste módulo.

A. Descrição VHDL do bloco *Serial Receiver*

Serial Control

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity SerialControl is
5  port( SS,clk,accept,eq5,reset : IN STD_LOGIC;
6        clr, wr, DXval, busy : OUT STD_LOGIC
7  );
8  end SerialControl;
9
10 architecture arq_SerialControl of SerialControl is
11
12 type STATE_TYPE is (READY, READING, WAITING,COMPLETED);
13
14 signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
15
16 begin
17
18 -- Registo Current State
19
20 CURRENT_STATE <= READY when (reset = '1') else NEXT_STATE when rising_edge(clk);
21
22 -- Máquina de Estados
23
24 GenerateNextState:
25 process (CURRENT_STATE, SS, eq5, accept)
26 begin
27     case CURRENT_STATE is
28         when READY => if(SS = '0') then
29                         NEXT_STATE <= READING;
30                     else
31                         NEXT_STATE <= READY;
32                     end if;
33
34         when READING => if(eq5 = '0') then
35                         NEXT_STATE <= READING;
36                     else
37                         NEXT_STATE <= WAITING;
38                     end if;
39
40         when WAITING => if(SS = '1') then
41                         NEXT_STATE <= COMPLETED;
42                     else
43                         NEXT_STATE <= WAITING;
44                     end if;
45
46         when COMPLETED => if(accept <= '0') then
47                             NEXT_STATE <= COMPLETED;
48                         else
49                             NEXT_STATE <= READY;
50                         end if;
51
52     end case;
53 end process;
54
55 -- Outputs
56 clr <= '1' when (CURRENT_STATE = READY) else '0';
57 wr <= '1' when (CURRENT_STATE = READING) else '0';
58
59 DXval <= '1' when (CURRENT_STATE = COMPLETED) else '0';
60
61 busy <= '1' when (CURRENT_STATE = COMPLETED) else '0';
62
63
64 end arq_SerialControl;

```

Counter

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY COUNTER_3 IS
5      PORT(
6          CLK : in std_logic;
7          E : in std_logic;
8          CLR: in std_logic;
9          R : out std_logic_vector (2 downto 0) :=(others => '0')
10         );
11  END COUNTER_3;
12
13
14  ARCHITECTURE arq_COUNTER OF COUNTER_3 IS
15
16
17      COMPONENT REGISTOR_RB IS
18          PORT( R : in std_logic_vector(2 downto 0);
19              CLR : in std_logic;
20              CL : in std_logic;
21              E : in std_logic;
22              TC : out std_logic;
23              F : out std_logic_vector (2 downto 0)
24             );
25      END COMPONENT;
26
27
28      COMPONENT SOMADOR3
29          PORT( A : in std_logic_vector(2 downto 0):=(others => '0');
30              B : in std_logic_vector(2 downto 0);
31              CI : in std_logic;
32              R : out std_logic_vector (2 downto 0):=(others => '0')
33             );
34      END COMPONENT;
35
36      SIGNAL SR: std_logic_vector(2 downto 0):=(others => '0');
37      SIGNAL RS: std_logic_vector(2 downto 0):=(others => '0');
38
39
40
41      BEGIN
42
43
44      USOMADOR : SOMADOR3 port map (
45          A => RS,
46          B(0) => '1',
47          B(1) => '0',
48          B(2) => '0',
49          CI => '0',
50          R => SR
51      );
52
53
54      UREGISTOR : REGISTOR_RB port map (
55          R => SR,
56          CL => CLK,
57          E => E,
58          F => RS,
59          CLR => CLR
60      );
61
62      R <= RS;
63  END arq_COUNTER;

```

Shift Register

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity ShiftRegister_SR is
5  port( Sin, CLK, enable, RST: in STD_LOGIC;
6        D : OUT STD_LOGIC_VECTOR(4 downto 0)
7  );
8  end ShiftRegister_SR;
9
10 architecture arq_ShiftRegister_SR of ShiftRegister_SR is
11
12 component ffd
13
14 port(CLK : in std_logic;
15       RESET : in STD_LOGIC;
16       SET : in std_logic;
17       D : IN STD_LOGIC;
18       EN : IN STD_LOGIC;
19       Q : out std_logic
20 );
21 end component;
22
23 signal DSignal: STD_LOGIC_VECTOR(4 downto 0);
24
25 begin
26
27 D(0)<=DSignal(4);
28 D(1)<=DSignal(3);
29 D(2)<=DSignal(2);
30 D(3)<=DSignal(1);
31 D(4)<=DSignal(0);
32
33 Uffd0 : ffd port map (
34     CLK => CLK,
35     RESET => RST,
36     SET => '0',
37     D => Sin,
38     EN => enable,
39     Q => DSignal(0)
40 );
41
42 Uffd1 : ffd port map (
43     CLK => CLK,
44     RESET => RST,
45     SET => '0',
46     D => DSignal(0),
47     EN => enable,
48     Q => DSignal(1)
49 );
50
51 Uffd2 : ffd port map (
52     CLK => CLK,
53     RESET => RST,
54     SET => '0',
55     D => DSignal(1),
56     EN => enable,
57     Q => DSignal(2)
58 );
59
60 Uffd3 : ffd port map (
61     CLK => CLK,
62     RESET => RST,
63     SET => '0',
64     D => DSignal(2),
65     EN => enable,
66     Q => DSignal(3)
67 );
68
69 Uffd4 : ffd port map (
70     CLK => CLK,
71     RESET => RST,
72     SET => '0',
73     D => DSignal(3),
74     EN => enable,
75     Q => DSignal(4)

```

```

76 );
77
78
79 end arq_ShiftRegister_SR;

```

Serial Receiver

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity SerialReceiver is
5  port(
6      SDX, SCLK, SS, accept, MCLK, reset : in std_logic;
7      DXval, busy : out std_logic;
8      data : out std_logic_vector (4 downto 0)
9  );
10
11  end SerialReceiver;
12
13  architecture arq_SerialReceiver OF SerialReceiver IS
14
15
16  component COUNTER_3
17  PORT(
18      CLK : in std_logic;
19      E: in std_logic;
20      CLR: in std_logic;
21      R : out std_logic_vector (2 downto 0) :=(others => '0')
22  );
23  end component;
24
25
26  component ShiftRegister_SR
27  port( Sin, CLK, enable, RST: in STD_LOGIC;
28      D : OUT STD_LOGIC_VECTOR(4 downto 0)
29  );
30  end component;
31
32
33  component equalTo5
34  port( D : IN STD_LOGIC_VECTOR(2 downto 0);
35      F : OUT STD_LOGIC
36  );
37  end component;
38
39
40  component SerialControl
41  port( SS,clk,accept,eq5,reset : IN STD_LOGIC;
42      clr, wr, DXval, busy : OUT STD_LOGIC
43  );
44  end component;
45
46
47
48  signal wrSignal, clrSignal, eq5Signal, Clk_signal : STD_LOGIC;
49  signal counterSignal : std_logic_vector(2 downto 0);
50
51  begin
52
53
54  uSerialControl : SerialControl port map(
55      SS => SS,
56      clk => MCLK,
57      accept => accept,
58      wr => wrSignal,
59      clr => clrSignal,
60      DXval => DXval,
61      reset => reset,
62      eq5 => eq5Signal,
63      busy => busy
64  );
65

```

```
66  uShiftRegister : ShiftRegister_SR port map(  
67      Sin => SDX,  
68      CLK => SCLK,  
69      enable => wrSignal,  
70      RST => reset,  
71      D => data  
72  );  
73  
74  uCOUNTER_3 : COUNTER_3 port map(  
75      CLK => SCLK,  
76      E => wrSignal,  
77      CLR => clrSignal,  
78      R => counterSignal  
79  );  
80  
81  uequalTo5 : equalTo5 port map (  
82      D=>counterSignal,  
83      F=>eq5Signal  
84  );  
85  
86  end arq_SerialReceiver;
```


B. Descrição VHDL do bloco *Dispatcher*

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Dispatcher is
5  port( Dval,clk,reset, Eq12 : IN STD_LOGIC;
6        WrL, done, enable, clr: OUT STD_LOGIC;
7        Din : IN STD_LOGIC_VECTOR(4 downto 0);
8        Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
9  );
10 end Dispatcher;
11
12 architecture behavioral of Dispatcher is
13
14
15
16
17 type STATE_TYPE is (WAITING, COUNTING,COMPLETED);
18
19
20 signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
21
22 begin
23
24
25
26
27 --   Registo Current State
28
29 CURRENT_STATE <= WAITING when (reset = '1') else NEXT_STATE when rising_edge(clk);
30
31 --   Máquina de Estados
32
33 GenerateNextState:
34 process (CURRENT_STATE, Dval, Eq12)
35     begin
36         case CURRENT_STATE is
37             when WAITING      => if(Dval = '1') then
38                                     NEXT_STATE      <= COUNTING;
39                                 else
40                                     NEXT_STATE      <= WAITING;
41                                 end if;
42
43             when COUNTING     => if(Eq12 = '1') then
44                                     NEXT_STATE      <= COMPLETED;
45                                 else
46                                     NEXT_STATE      <= COUNTING;
47                                 end if;
48
49             when COMPLETED   => if(Dval = '0') then
50                                     NEXT_STATE      <= WAITING;
51                                 else
52                                     NEXT_STATE      <= COMPLETED;
53                                 end if;
54
55         end case;
56
57     end process;
58
59 --   Outputs
60 WrL <= '1' when (CURRENT_STATE = COUNTING) else '0';
61 done <= '1' when (CURRENT_STATE = COMPLETED) else '0';
62 clr <= '1' when (CURRENT_STATE = WAITING) else '0';
63
64 Dout <= Din when (CURRENT_STATE = COUNTING);
65
66 end behavioral;

```

C. Descrição VHDL do bloco SLCDC

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY SLCDC IS
5      PORT( MCLK,reset : IN STD_LOGIC;
6            NOT_SS, SCLK, SDX: IN STD_LOGIC; --software
7            WrL : OUT STD_LOGIC;
8            Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
9      );
10 END SLCDC;
11
12
13 ARCHITECTURE arq_SLCDC OF SLCDC IS
14
15     component COUNTER
16         PORT( CLK : in std_logic;
17               E : in std_logic;
18               clr: in std_logic;
19               R : out std_logic_vector (3 downto 0)
20         );
21     end component;
22
23
24
25     component equalTo12Dispatcher
26     port( D : IN STD_LOGIC_VECTOR(3 downto 0);
27           F : OUT STD_LOGIC
28     );
29     end component;
30
31
32     COMPONENT SerialReceiver
33     port(
34         SDX, SCLK, SS, accept, MCLK, reset : in std_logic;
35         DXval, busy : out std_logic;
36         data : out std_logic_vector (4 downto 0)
37     );
38 END COMPONENT;
39
40     COMPONENT Dispatcher
41     port( Dval,clk,reset, Eq12 : IN STD_LOGIC;
42           WrL, done, clr : OUT STD_LOGIC;
43           Din : IN STD_LOGIC_VECTOR(4 downto 0);
44           Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
45     );
46 END COMPONENT;
47
48     COMPONENT CLKDIV is
49         generic(div: natural := 50000000);
50         port ( clk_in: in std_logic;
51               clk_out: out std_logic);
52     END COMPONENT;
53
54     signal DXvalSignal, SCLKSignal, MCLKDivSignal, acceptDoneSignal, eq12Signal, WrLSignal,
55     enableSignal,clrSignal : STD_LOGIC;
56     signal DataSignal : STD_LOGIC_VECTOR (4 downto 0);
57     signal counterSignal : STD_LOGIC_VECTOR (3 downto 0);
58
59 begin
60     WrL <= WrLSignal;
61
62     --uCLKDIV : CLKDIV generic map(2) port map(
63         -- clk_in => MCLK,
64         -- clk_out => MCLKDivSignal
65     --);
66
67
68     UCOUNTER: COUNTER port map(
69         Clk => MCLK,--MCLKDivSignal,
70         E => WrLSignal,
71         clr => clrSignal,
72         R => CounterSignal
73     );
74

```

```
75 uequalTo12Dispatcher : equalTo12Dispatcher port map (  
76     D=>counterSignal,  
77     F=>eq12Signal  
78 );  
79  
80 uSerialReceiver: SerialReceiver PORT MAP (  
81     SDX    => SDX,  
82     SCLK   => SCLK,  
83     SS     => NOT_SS,  
84     accept => acceptDoneSignal,  
85     MCLK   => MCLK,--MCLKDivSignal,  
86     reset  => reset,  
87     DXval  => DXvalSignal,  
88     data   => DataSignal  
89 );  
90  
91 uDispat: Dispatcher PORT MAP (  
92     Dval  => DXvalSignal,  
93     clk   => MCLK,--MCLKDivSignal,  
94     reset => reset,  
95     WrL   => WrLSignal,  
96     done  => acceptDoneSignal,  
97     Din   => DataSignal,  
98     Dout  => Dout,  
99     Eq12  => eq12Signal,  
100     clr  => clrSignal  
101  
102 );  
103  
104  
105  
106  
107 end arq_SLCDC;  
108  
109
```

D. Descrição VHDL do bloco *SLCDC_USBPORT*

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY SLCDC_USBPORT IS
5      PORT(
6
7          MCLK,reset : IN STD_LOGIC;
8          WrL , WrLED, SDX,SCLK : OUT STD_LOGIC;
9          Dout : OUT STD_LOGIC_VECTOR(4 downto 0);
10         LDout : OUT STD_LOGIC_VECTOR(4 downto 0)
11
12     );
13 END SLCDC_USBPORT;
14
15
16
17
18
19 ARCHITECTURE arq_SLCDC_USBPORT OF SLCDC_USBPORT IS
20
21     COMPONENT UsbPort
22     PORT
23     (
24         inputPort: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
25         outputPort : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
26     );
27 END COMPONENT;
28
29     COMPONENT SLCDC
30     PORT( MCLK,reset : IN STD_LOGIC;
31         NOT_SS, SCLK, SDX: IN STD_LOGIC; --software
32         WrL : OUT STD_LOGIC;
33         Dout : OUT STD_LOGIC_VECTOR(4 downto 0)
34     );
35 END COMPONENT;
36
37
38     COMPONENT CLKDIV is
39         generic(div: natural := 50000000);
40         port ( clk_in: in std_logic;
41             clk_out: out std_logic);
42     END COMPONENT;
43
44
45
46     signal UsbPortInputSignal, UsbPortOutputSignal : STD_LOGIC_VECTOR (7 downto 0);
47     signal MCLKDivSignal, WrLSignal: STD_LOGIC;
48     signal DoutSignal : STD_LOGIC_VECTOR (4 downto 0);
49
50     begin
51
52         --uCLKDIV : CLKDIV port map(
53             -- clk_in => MCLK,
54             -- clk_out => MCLKDivSignal
55         --);
56
57         uUsbPort: UsbPort PORT MAP(
58             inputPort => UsbPortInputSignal,
59             outputPort => UsbPortOutputSignal
60

```

```
61 );
62
63
64 uSLCDC: SLCDC PORT MAP(
65     MCLK    => MCLK,
66     reset    => reset,
67     NOT_SS   => UsbPortOutputSignal(3), --0x08
68     SCLK     => UsbPortOutputSignal(1), --0x02
69     SDX      => UsbPortOutputSignal(0), --0x01
70     WrL      => WrLSignal,
71     Dout     => DoutSignal
72
73 );
74
75 SDX <= UsbPortOutputSignal(0); --0x01;
76 SCLK <= UsbPortOutputSignal(1); --0x02;
77 LDout <= DoutSignal;
78 Dout <= DoutSignal;
79 WrL <= WrLSignal;
80 WrLED <= WrLSignal;
81
82 end arch SLCDC USBPORT;
```

E. Atribuio de pinos do mdulo *SLDC_USBPORT*

```
#=====
# CLOCK
#=====

set_location_assignment PIN_P11 -to MCLK

#=====
# SW
#=====

set_location_assignment PIN_C10 -to reset


#=====
#LCD
#=====

set_location_assignment PIN_W8 -to Dout[0]
set_location_assignment PIN_V5 -to WrL


set_location_assignment PIN_W11 -to Dout[1]
set_location_assignment PIN_AA10 -to Dout[2]
set_location_assignment PIN_Y8 -to Dout[3]
set_location_assignment PIN_Y7 -to Dout[4]


#=====
# LED
#=====

set_location_assignment PIN_A8 -to LDout[0]
set_location_assignment PIN_A9 -to WrLED
set_location_assignment PIN_A10 -to LDout[1]
set_location_assignment PIN_B10 -to LDout[2]
set_location_assignment PIN_D13 -to LDout[3]
set_location_assignment PIN_C13 -to LDout[4]
#set_location_assignment PIN_E14 -to LEDR[6]
#set_location_assignment PIN_D14 -to LEDR[7]
set_location_assignment PIN_A11 -to SDX
set_location_assignment PIN_B11 -to SCLK


#=====
# End of pin and io_standard assignments
#=====
```

F. C3digo Kotlin - HAL

```
object HAL {
    var written = 0b0000_0000
    private var ACTIVE = false
    fun init() { // Inicia a classe
        if(!ACTIVE) {
            UsbPort.write(written)
            ACTIVE=true
        }
    }

    // Retorna true se o bit tiver o valor l3gico '1'
    fun isBit(mask: Int): Boolean = (mask and UsbPort.read()) != 0

    // Retorna os valores dos bits representados por mask presentes no UsbPort
    fun readBits(mask: Int): Int = mask and UsbPort.read()

    // Escreve nos bits representados por mask o valor de value
    /**
     * value -> 0000_1001.
     * mask -> 0000_1111.
     * lastWritten -> 1111_0111.
     * new lastWritten -> 1111_1001.
     * 1º: (value and mask) -> 0000_1001 sets the bits in value to be written to the ones in the
     mask.
     * 2º: (lastWritten and mask.inv()) -> 1111_0000 sets the bits in lastWritten that are not
     in the mask,this operation
     *     sets to 0 all the bits in lastWritten that are not in the mask, preparing it to
     receive the updated value.
     * 3º: (value and mask) or (lastWritten and mask.inv()) -> 0000_1001 or 1111_0000 ->
     1111_1001 sets the bits in
     *     lastWritten that are in the mask to the corresponding bits in value and keeps the
     bits that are not in the mask unchanged.
     */

    fun writeBits(mask: Int, value: Int) {
        written = (value and mask) or (written and mask.inv())
        UsbPort.write(written)
    }

    // Coloca os bits representados por mask no valor l3gico '1'
    fun setBits(mask: Int) {
        written = (written or mask)
        UsbPort.write(written)
    }

    // Coloca os bits representados por mask no valor l3gico '0'
    fun clrBits(mask: Int) {
        written = written and mask.inv()
        UsbPort.write(written)
    }
}
```

G. Código Kotlin – Serial Emitter

```
/**
 * Mapeamento
 *   n       7   6   5   4   3   2   1   0
 * inputPort :BSY  0   0   0   0   0   0   0   //inputPort(n)
 * outPort   : 0   0   0   0   LCD DOOR SCLK SDX //outputPort(n)
 *
 *               SS   SS
 * D[0:4] :    -   -   -   D(3) D(2) D(1) D(0) RS
 */

object SerialEmitter {    // Envia tramas para os diferentes módulos Serial Receiver
    enum class Destination {LCD, DOOR}
    private const val MASK_BUSY = 0x80
    private const val MASK_NOT_SS_LCD = 0x08
    private const val MASK_NOT_SS_DOOR = 0x04
    private const val MASK_SCLK = 0x02
    private const val MASK_SDx = 0x01
    private const val DATA_SIZE = 5

    // Inicia a classe
    fun init() {
        HAL.init()
        HAL.setBits(MASK_NOT_SS_LCD) // SS = 1
        HAL.setBits(MASK_NOT_SS_DOOR) // SS = 1
        HAL.clrBits(MASK_SCLK) // SCLK = 0
        HAL.clrBits(MASK_SDx) // SDx = 0
    }

    // Envia uma trama para o SerialReceiver identificado o destino em addr e os bits de dados em 'data'.
    fun send(addr: Destination, value: Int) {
        var data = value
        while (isBusy()) { }
        val address = if (addr == Destination.LCD) MASK_NOT_SS_LCD else MASK_NOT_SS_DOOR
        for (i in 0 until DATA_SIZE) {
            HAL.clrBits(MASK_SCLK) // SCLK = 0
            HAL.clrBits(address) // SS = 0
            HAL.writeBits(0x01, 0x01 and data) // SDx = data[0]
            data = data shr 1 // data = data >> 1 to send bit a bit
            HAL.setBits(MASK_SCLK) // SCLK = 1
        }
        HAL.clrBits(0x01) // SDx = 0
        HAL.clrBits(MASK_SCLK) // SCLK = 0
        HAL.setBits(address) // SS = 1
    }

    // Retorna true se o canal série estiver ocupado
    fun isBusy(): Boolean = HAL.isBit(MASK_BUSY)
}
```


H. Código Kotlin – LCD

```
/**
 * LCD 16*2
 * Display positions
 *
 * 1ª line: 0x00 to 0x0F
 * 2ª line: 0x40 to 0x4F
 *
 * DDRAM : Display data RAM
 * CGRAM : Character generator RAM
 * ACG : CGRAM address
 * ADD : DDRAM address (cursor address)
 * AC : address counter used for DD and CGRAM addresses
 * DDRAM 0 0 1 ADD ADD ADD ADD ADD ADD
 *
 */
object LCD {
    // Escreve no LCD usando a interface a 4bits
    private const val LINES = 2
    const val COLS = 16 // Dimensão do display.
    private const val DISPLAY_ON = 0xF //Mascara para ligar o display,
    private const val DISPLAY_OFF = 0x8 //Mascara para desligar o display
    private const val DISPLAY_SET = 0x3 //Function set
    private const val MASK_ENTRYMODE = 0x6 //Mascara para entry mode
    private const val DISPLAY_SET_NIBBLE = 0x2 //set 4 bits
    private const val MASK_PARALLEL_RS = 0x10 //Mascara para o bit de RS
    private const val MASK_LOW_DATA = 0x0F //Mascara para os 4 bits menos significativos
    private const val MASK_HIGH_DATA = 0xF0 //Mascara para os 4 bits mais significativos
    private const val DISPLAY_CLEAR : Int = 0x1 //Mascara para instrução de limpar o display
    private const val DISPLAY_CONFIG :Int=0x28//Mascara para configurar as linhas e a fonte do LCD

    // Escreve um nibble de comando/dados no LCD em paralelo
    //data -> d3..d0, recebe os quatro bits de menor peso
    private fun writeNibbleParallel(rs: Boolean, data: Int){
        if (rs) {
            HAL.setBits(MASK_PARALLEL_RS) //RS = 1
        } else {
            HAL.clrBits(MASK_PARALLEL_RS)//RS = 0
        }
        HAL.writeBits(MASK_LOW_DATA, data) //d3..d0
    }

    // Escreve um nibble de comando/dados no LCD em série
    private fun writeNibbleSerial(rs: Boolean, data: Int) {
        var d = data
        if (rs) d = (data shl 1) or 0x01 else d = (d shl 1) or 0x00
        SerialEmitter.send(SerialEmitter.Destination.LCD, d)
    }

    // Escreve um nibble de comando/dados no LCD
    private fun writeNibble(rs: Boolean, data: Int) {
        writeNibbleSerial(rs,data)
    }
}
```

```
}

// Escreve um byte de comando/dados no LCD
private fun writeByte(rs: Boolean, data: Int) {
    writeNibble(rs, (MASK_HIGH_DATA and data) shr 4)
    writeNibble(rs, MASK_LOW_DATA and data)
}

// Escreve um comando no LCD
private fun writeCMD(data: Int) {
    writeByte(false, data)
}

// Escreve um dado no LCD
private fun writeDATA(data: Int) {
    writeByte(true, data)
}

// Envia a sequência de iniciação para comunicação a 4 bits.
fun init() {
    SerialEmitter.init()
    Time.sleep(15)
    writeNibble(false, DISPLAY_SET)
    Time.sleep(5)
    writeNibble(false, DISPLAY_SET)
    Time.sleep(1)
    writeNibble(false, DISPLAY_SET)
    writeNibble(false, DISPLAY_SET_NIBBLE)
    // Function Set, interface a 4 bits
    writeCMD(DISPLAY_CONFIG) // define N:1, F:0
    writeCMD(DISPLAY_OFF) // display off
    writeCMD(DISPLAY_CLEAR) // clear
    writeCMD(MASK_ENTRYMODE) // define I/D:1, S:0
    writeCMD(DISPLAY_ON) // display on
}

// Escreve um caracter na posição corrente.
fun write(c: Char) =
    writeDATA(c.code)

// Escreve uma string na posição corrente.
fun write(text: String) {
    for (c in text) {
        write(c)
    }
}

// Envia comando para posicionar cursor ('line':0..LINES-1 , 'column':0..COLS-1) fun
cursor(line: Int, column: Int) ...
fun cursor(line: Int, column: Int): Unit {
    if (line >= LINES || line < 0 || column >= COLS || column < 0) return
    writeCMD((line * 0x40 + column) or 0x80)
}
```

```
// Envia comando para limpar o ecrã e posicionar o cursor em (0,0)
fun clear() {
    writeCMD(DISPLAY_CLEAR)
    cursor(0,0)
}

}
```