

O módulo *Keyboard Reader* é constituído por três blocos principais: i) o decodificador de teclado (*Key Decode*); ii) o bloco de armazenamento (designado por *Ring Buffer*); e iii) o bloco de entrega ao consumidor (designado por *Output Buffer*). Neste caso o módulo *Control*, implementado em *software*, é a entidade consumidora.


 



Figura 1 – Diagrama de blocos do módulo *Keyboard Reader*

1 Key Decode

O bloco *Key Decode* implementa um decodificador de um teclado matricial 4x3 por *hardware*, sendo constituído por três sub-blocos: i) um teclado matricial de 4x3; ii) o bloco *Key Scan*, responsável pelo varrimento do teclado; e iii) o bloco *Key Control*, que realiza o controlo do varrimento e o controlo de fluxo, conforme o diagrama de blocos representado na Figura 2a. O controlo de fluxo de saída do bloco *Key Decode* (para o módulo *Key Buffer*), define que o sinal K_{val} é ativado quando é detetada a pressão de uma tecla, sendo também disponibilizado o código dessa tecla no barramento $K_{0:3}$. Apenas é iniciado um novo ciclo de varrimento ao teclado quando o sinal K_{ack} for ativado e a tecla premida for libertada. O diagrama temporal do controlo de fluxo está representado na Figura 2b.

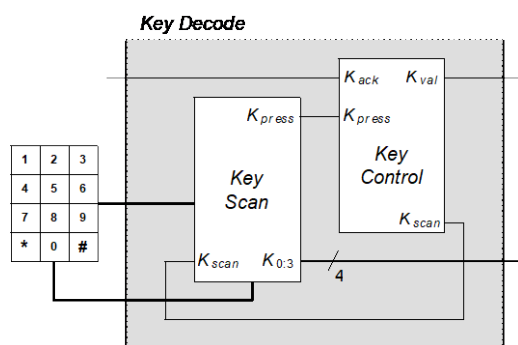

a) Diagrama de blocos

 

b) Diagrama temporal

Figura 2 – Bloco *Key Decode*

O bloco *Key Scan* foi implementado de acordo com o diagrama de blocos representado na Figura 3. Na

implementação do bloco *Key Scan* optámos pelo diagrama de blocos *versão 1*, uma vez que na *versão 2* o *Kpress* fica ativo, se uma tecla for premida, independentemente da linha que esteja a ser observada.

Na versão 1, de acordo com a figura 3 este é constituído por um decoder (2 por 3), um multiplexer (4 por 1) e um contador de 4 bits que é responsável pela seleção das saídas do decoder e das entradas do multiplexer.

Às entradas do multiplexer estão ligadas as linhas do teclado de forma a ativar o *Kpress* quando uma tecla na linha seleccionada seja premida. Nas saídas do decoder encontram-se as colunas do teclado, de forma a seleccionar uma linha. Quando uma tecla é premida a entrada enable do contador recebe o valor lógico 0, para que seja possível fazer a leitura do código da tecla premida, sendo os bits de maior peso a coluna da tecla foi premida e os bits de menor peso a linha da tecla premida.

O bloco *Key Control* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 4.

No estado 00 o *Kscan* está ativo de forma a fazer o varrimento do teclado até que uma tecla seja premida, sendo essa avaliação feita através do sinal *Kpress*. Quando uma tecla é premida entramos no estado 01 e o sinal *Kval* fica ativo indicando que foi pressionada uma tecla válida, e mantém-se neste estado até que o sinal *Kack* fique ativo indicando que a leitura do código da tecla está completa e foi aceite. Quando *Kack* ficar ativo saímos do estado e entramos no estado 10, a aguardar que o sinal *Kack* e o sinal *Kpress* estejam desativados de forma que apenas seja iniciado um novo varrimento do teclado quando o sinal *Kack* esteja desativado e a tecla premida for libertada.

A descrição hardware do bloco *Key Decode* em VHDL encontra-se no Anexo A.

 


Figura 3 - Diagrama de blocos do bloco *Key Scan*

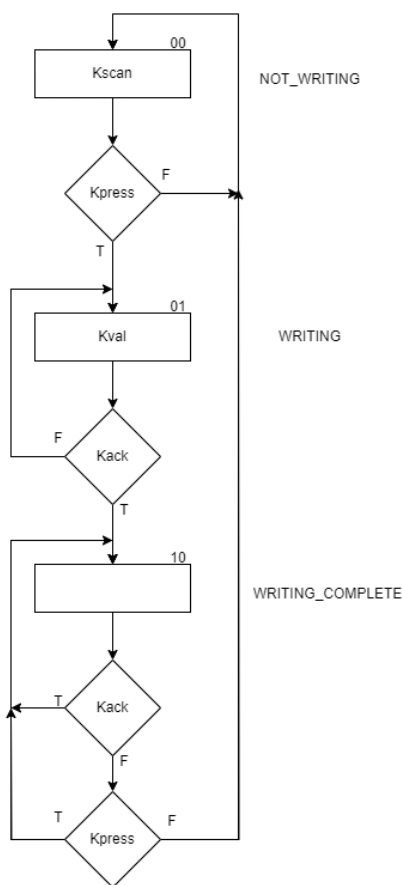


Figura 4 – Máquina de estados do bloco *Key Control*

Com base nas descrições do bloco *Key Decode* implementou-se parcialmente o módulo *Keyboard Reader* de acordo com o esquema elétrico representado no Anexo D.

2 Ring Buffer

O bloco RingBuffer é uma estrutura de dados para armazenamento de teclas com disciplina FIFO (First In First Out), com capacidade de armazenar até oito palavras de quatro bits. A escrita de dados no Ring Buffer inicia-se com a ativação do sinal DAV (Data Available) pelo sistema produtor, neste caso pelo Key Decode, indicando que tem dados para serem armazenados. Logo que tenha disponibilidade para armazenar informação, o Ring Buffer escreve os dados D0:3 em memória. Concluída a escrita em memória ativa o sinal DAC (Data Accepted) para informar o sistema produtor que os dados foram aceites. O sistema produtor mantém o sinal DAV ativo até que DAC seja ativado. O Ring Buffer só desativa DAC depois de DAV ter sido desativado. A implementação do Ring Buffer é baseada numa memória RAM (Random Access Memory). O endereço de escrita/leitura, selecionado por *putget* é definido pelo bloco Memory Address Control

(MAC) composto por dois registos, que contêm o endereço de escrita e leitura, designados por *putIndex* e *getIndex* respetivamente. O MAC suporta assim ações de *incPut* e *incGet*, gerando informação se a estrutura de dados está cheia (Full) ou se está vazia (Empty). O bloco Ring Buffer procede à entrega de dados à entidade consumidora, sempre que esta indique que está disponível para receber, através do sinal Clear To Send (CTS). Na Figura 5 é apresentado o diagrama de blocos para uma estrutura do bloco Ring Buffer.

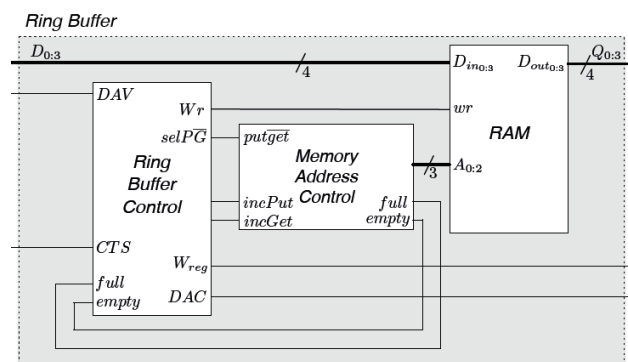


Figura 5 Diagrama de blocos do bloco Ring Buffer

No desenvolvimento do bloco Ring Buffer começou-se por desenvolver o bloco Memory Address Control de acordo com as informações fornecidas. Desta forma foi necessário recorrer a 2 contadores de 3 bits, uma vez que a RAM presente no diagrama de blocos tem 8 endereços disponíveis, para incrementar os endereços de leitura e escrita designados por *putIndex* e *getIndex* respetivamente.

Para gerar a informação dos sinais Full e Empty foi usado um contador crescente/decrescente que opera quando o MAC recebe os sinais *incput* ou *incGet*, a contagem crescente ou decrescente é determinada pelo sinal *incPut* sendo crescente quando este tem o valor lógico '1' e decrescente quando tem o valor lógico '0', de forma a acompanhar o número de endereços ocupados com informação que não foi enviada para leitura.

Os endereços de leitura e escrita são fornecidos à RAM por um multiplexer 2 por 1, onde a seleção da entrada recebe o sinal *putget*, quando este tem o valor lógico '0' é enviado o *idxGet* e quando este apresenta o valor lógico '1' é enviado o *idxPut*.

Em baixo encontra-se o diagrama de blocos do bloco MAC.

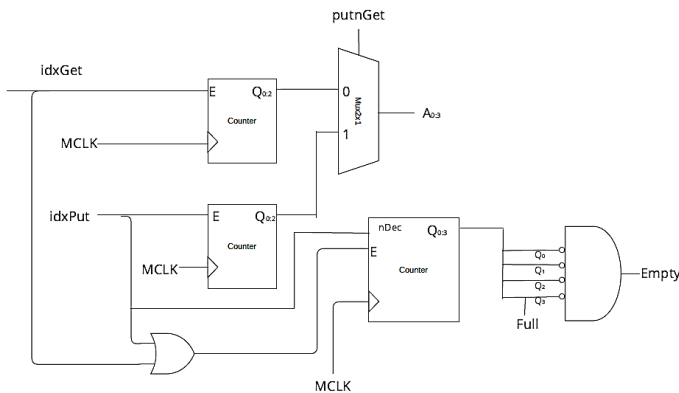


Figura 6 Diagrama de blocos do bloco MAC

O bloco *Ring Buffer Control* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 7.

No estado 00 aguarda-se uma instrução de escrita ou leitura, no caso da instrução recebida seja de escrita, com a ativação do sinal DAV, é verificando antes de realizar a escrita na RAM, se esta tem algum endereço disponível para armazenar dados. Se os endereços da RAM estiverem todos ocupados, entramos no estado 10 onde é realizada uma espera pela ativação do sinal CTS, de forma a realizar uma leitura da RAM, libertando espaço de forma a concluir a instrução de leitura. Quando o sinal CTS estiver ativo, ocorre a passagem para o estado 101, onde é ativado o sinal *Wreg* de forma a registar os dados lidos. Depois de enviar os dados para o bloco Output Buffer no estado 111 o sinal *incGet* é ativado de forma a incrementar o *idxGet* e verifica-se se estava a ser executada uma instrução de escrita, de forma a concluir a mesma. A instrução de escrita é realizada ativando o sinal *selPG* de forma a fornecer o endereço à RAM, no estado seguinte é ativado o sinal *Wr* de forma a escrever os dados recebidos na RAM, depois da escrita é incrementado o *idxPut* com a ativação do sinal *incPut* e a seguir passamos para o estado 110 onde o sinal *DAC* é ativado de forma a informar o bloco Key Decode que os dados recebidos foram aceites.

No caso de o sinal *full* não esteja ativo é realizada a instrução de escrita, sem realizar uma instrução de leitura.

Quando sinal *DAV* não estiver ativo, mas o sinal *CTS* tenha o valor lógico 1, verifica-se se a RAM está vazia através do sinal *empty*. Se a RAM não tem dados para leitura mantém-se no estado 00, caso contrário ocorre a passagem para o estado 101 e é realizada a operação de leitura tal como descrita anteriormente.

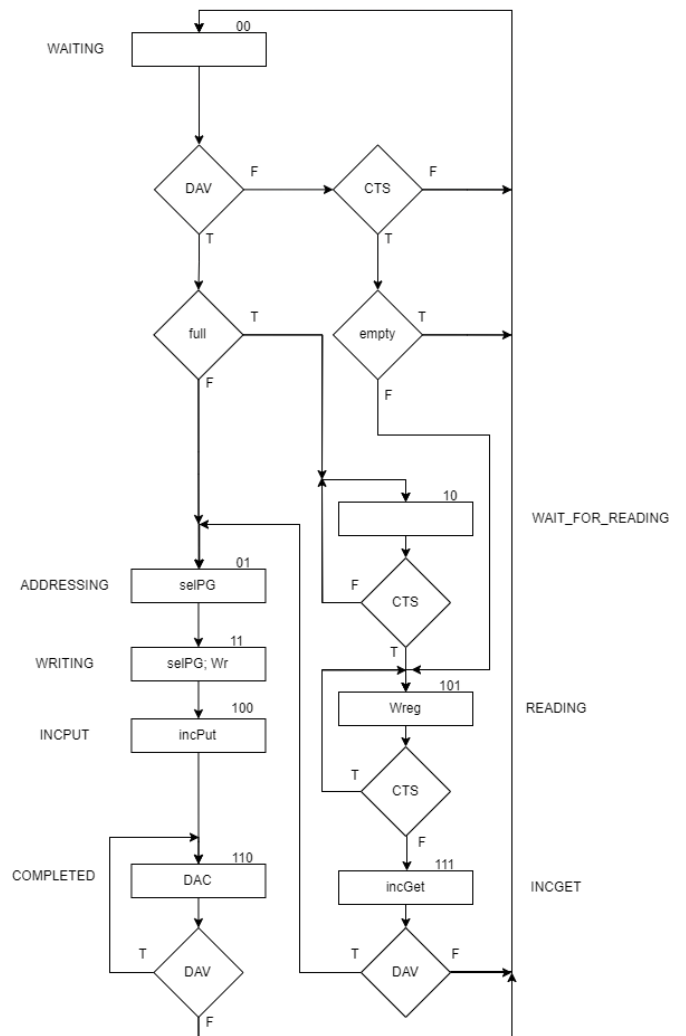


Figura 7 Máquina de estados do bloco Ring Buffer Control

A descrição hardware do bloco *Ring Buffer* em VHDL encontra-se no Anexo B.

3 Output Buffer

O bloco Output Buffer do Keyboard Reader é responsável pela interação com o sistema consumidor, neste caso o módulo Control. O Output Buffer indica que está disponível para armazenar dados através do sinal *OBfree*. Assim, nesta situação o sistema produtor pode ativar o sinal *Load* para registar os dados. O Control quando pretende ler dados do Output Buffer, aguarda que o sinal *Dval* fique ativo, recolhe os dados e pulsa o sinal *ACK* indicando que estes já foram consumidos. O Output Buffer, logo que o sinal *ACK* pulse, deve invalidar os dados baixando o sinal *Dval* e sinalizar que está novamente disponível para entregar dados ao sistema consumidor, ativando o sinal *OBfree*. Na Figura 8, é apresentado o diagrama de blocos do Output Buffer.

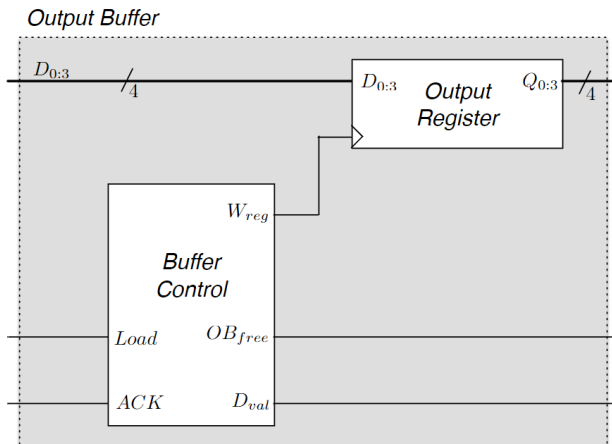



Figura 8 Diagrama de blocos do bloco Output Buffer

Sempre que o bloco emissor Ring Buffer tenha dados disponíveis e o bloco de entrega Output Buffer esteja disponível (OBfree ativo), o Ring Buffer realiza uma leitura da memória e entrega os dados ao Output Buffer ativando o sinal Wreg. O Output Buffer indica que já registou os dados desativando o sinal OBFree.

Figura 9 Máquina de estados do bloco Buffer Control

O bloco *Buffer Control* foi implementado pela máquina de estados representada em *ASM-chart* na Figura 8.

A máquina de estados do bloco Buffer Control inicialmente encontra-se no estado 00, com o sinal OBfree indicando que está disponível para receber dados, quando o sinal Load tiver o valor lógico '1' (indicando que o bloco Ring Buffer tem dados para entregar) ocorre a passagem para o estado 01 onde o sinal Wreg é ativado de forma a realizar a escrita no bloco Output Register e a seguir ocorre a passagem para o estado 10 onde o sinal Dval é ativado (informando o Control de que tem dados disponíveis para recolha) e mantém-se ativo até que o sinal ACK tenha o valor lógico '1', indicando que os dados foram consumidos pelo Control. Por fim invalida os dados baixando o sinal Dval e sinalizar que está novamente disponível para entregar dados ao sistema consumidor, ativando o sinal OBfree.

 

A descrição hardware do bloco *Output Buffer* em VHDL encontra-se no Anexo C.

4 Interface com o Control

Implementou-se o módulo *Control* em *software*, recorrendo a linguagem *Kotlin* e seguindo a arquitetura lógica apresentada na Figura 8.

 


Figura 10 – Diagrama lógico do módulo *Control* de interface com o módulo *Keyboard Reader*

HAL e *KBD* desenvolvidos são descritos nas secções 3.1. e 3.2, e o código fonte desenvolvido nos Anexos C e D, respetivamente.

4.1 HAL

A classe HAL é responsável por comunicar com o bloco UsbPort, fazendo a leitura e a escrita no bloco UsbPort.

De forma a evitar efetuar a leitura do bloco UsbPort repetidamente foi criada uma variável global (written) dentro da classe para guardar o último valor escrito.

Nesta classe temos a função init que inicia a classe, a função isBit() que retorna true se o bit passado na máscara tiver o valor lógico 1. A função readBits() efetua uma leitura tal como a função isBit() mas para um conjunto de bits.

A função writeBits() escreve um valor num conjunto de bits, a função setBits() escreve nos bits da máscara o valor lógico 1. E a função clrBits() coloca o valor lógico 0 no bit indicado na máscara.

4.2 KBD

Esta classe utiliza a classe HAL de forma a obter do bloco UsbPort um código de uma tecla e retornar o char equivalente ao código lido.

Nesta classe temos uma lista com os Char's correspondentes aos códigos possíveis, temos a função getKey() que retorna o char correspondente ao código da tecla premida imediatamente, quando o sinal Dval do bloco Output Buffer estiver ativo e ativa o sinal ACK do bloco

Control informando que os dados foram recebidos . E por fim temos a função waitKey() que retorna o char correspondente ao código da tecla premida ao fim de um intervalo de tempo ou NONE se não for premida nenhuma tecla.

5 Conclusões

O objetivo deste módulo é descodificar a tecla pressionada e enviar o respetivo código para o Control. Para isso, utilizamos funções previamente desenvolvidas para leitura de portas, que convertem o código recebido em carácter de forma a descodificar a tecla premida. Para além das funções dos objetos KBD e HAL, foi necessário realizar um contador que efetuasse a soma com o resultado presente nas suas saídas, por essa razão foi implementado um register que coloca o valor da saída do contador numa das entradas do mesmo, tendo em conta que em uma das entradas é introduzido o valor 1. Em relação ao software, este foi testado no simulador e aparenta ter um funcionamento correto, e os módulos Key Decode, Ring Buffer e Output Buffer também foram testados, primeiro no simulador e depois na placa onde mostraram um funcionamento correto.

A. Descrição VHDL do bloco *Key Decode*

Key Scan

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY KEY_SCAN IS
5      PORT( Kscan: in std_logic;
6            clr: in std_logic;
7            clk: in std_logic;
8            kpress : out std_logic;
9            KEYPAD_LIN : in std_logic_vector(3 downto 0);
10           KEYPAD_CODE: out std_logic_vector(3 downto 0);
11           KEYPAD_COL : out std_logic_vector(3 downto 0)
12       );
13  END KEY_SCAN;
14
15  ARCHITECTURE arq_KEY_SCAN OF KEY_SCAN IS
16
17      component DECODER2_3
18          PORT( S: in STD_LOGIC_VECTOR(1 downto 0);
19                A,B,C,D: out STD_LOGIC
20            );
21      end component;
22
23      component MUX4_1
24          PORT( A,B,C,D: in STD_LOGIC;
25                S: in STD_LOGIC_VECTOR(1 downto 0);
26                Y: out STD_LOGIC
27            );
28      end component;
29
30      component COUNTER
31          PORT( CLK : in std_logic;
32                E : in std_logic;
33                clr: in std_logic;
34                R : out std_logic_vector (3 downto 0)
35            );
36      end component;
37
38      signal Coluna, Linha: std_logic_vector (1 downto 0);
39      signal A , B : std_logic;
40
41  BEGIN
42
43      Kpress <= B;
44      A <= Kscan and (not B); -- 1 and not 0 => 1 , 1 and 0
45
46      KEYPAD_CODE(0) <= Linha(0);
47      KEYPAD_CODE(1) <= Linha(1);
48      KEYPAD_CODE(2) <= Coluna(0);
49      KEYPAD_CODE(3) <= Coluna(1);
50
51      UDECODER: DECODER2_3 port map(
52          S(0) => Coluna(0),
53          S(1) => Coluna(1),
54          A => KEYPAD_COL(0),
55          B => KEYPAD_COL(1),
56          C => KEYPAD_COL(2),
57          D => KEYPAD_COL(3)
58      );
59
60      UMUX4_1: MUX4_1 port map(
61          S(0) => Linha(0),
62          S(1) => Linha(1),
63          A => KEYPAD_LIN(0),
64          B => KEYPAD_LIN(1),
65          C => KEYPAD_LIN(2),
66          D => KEYPAD_LIN(3),
67          Y => B;
68      );
69
70      UCOUNTER: COUNTER port map(
71          clk => clk,
72          E => A,
73          clr => clr,
74          R(0) => Linha(0),
75          R(1) => Linha(1),
76          R(2) => Coluna(0),
77          R(3) => Coluna(1));
78
79  end arq_KEY_SCAN;

```

Key Control

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY KEY_CONTROL IS
5      PORT(
6          CLK : in std_logic;
7          Kack : in std_logic;
8          Kpress: in std_logic;
9          Reset: in std_logic;
10         Kval : out std_logic;
11         Kscan : out std_logic
12     );
13 END KEY_CONTROL;
14
15 architecture behavioral of KEY_CONTROL is
16
17     type STATE_TYPE is (STATE_NOT_WRITING, STATE_WRITING, STATE_WRITING_COMPLETE);
18     signal CurrentState, NextState : STATE_TYPE;
19
20 begin
21     -- Flip-Flop's
22     CurrentState <= STATE_NOT_WRITING when Reset = '1' else NextState when rising_edge(CLK);
23
24     --Generate Next State
25     GenerateNextState:
26     process(CurrentState, Kack, Kpress)
27     begin
28         case CurrentState is
29             when STATE_NOT_WRITING => if (Kpress = '1') then NextState <= STATE_WRITING;
30                                     else
31                                         NextState <= STATE_NOT_WRITING;
32                                     end if;
33             when STATE_WRITING => if (Kack = '1') then NextState <=
34                                     STATE_WRITING_COMPLETE;
35                                     else
36                                         NextState <= STATE_WRITING;
37                                     end if;
38             when STATE_WRITING_COMPLETE=> if (Kack = '0' and kpress = '0') then NextState <=
39                                     STATE_NOT_WRITING;
40                                     else
41                                         NextState <= STATE_WRITING_COMPLETE;
42                                     end if;
43         end case;
44     end process;
45
46     --Generate outputs
47     Kscan <= '1' when (CurrentState = STATE_NOT_WRITING) else '0';
48     Kval <= '1' when (CurrentState = STATE_WRITING) else '0';
49
50 end behavioral;

```


Key Decode

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Key_Decode is
5  port( Kack, CLK, Reset : IN STD_LOGIC;
6        Kval : OUT STD_LOGIC;
7        KEYPAD_LIN : in std_logic_vector(3 downto 0);
8        KEYPAD_CODE: out std_logic_vector(3 downto 0);
9        KEYPAD_COL : out std_logic_vector(3 downto 0)
10 );
11 end;
12
13 architecture arq_KeyDecode of Key_Decode is
14
15 component KEY_SCAN
16 port( Kscan, Clk, Clr : IN STD_LOGIC;
17       Kpress : OUT STD_LOGIC;
18       KEYPAD_LIN : in std_logic_vector(3 downto 0);
19       KEYPAD_CODE: out std_logic_vector(3 downto 0);
20       KEYPAD_COL : out std_logic_vector(3 downto 0)
21 );
22 end component;
23
24 component KEY_CONTROL
25 port( Kack,Kpress,CLK,Reset : IN STD_LOGIC;
26       Kval, Kscan : OUT STD_LOGIC
27 );
28 end component;
29
30 signal KscanSignal,KpressSignal : STD_LOGIC;
31
32 begin
33
34
35
36
37
38
39
40
41
42
43 uKeyScan : KEY_SCAN port map(
44     Kscan => KscanSignal,
45     Kpress => KpressSignal,
46     Clr => Reset,
47     Clk => CLK,
48     KEYPAD_LIN => KEYPAD_LIN,
49     KEYPAD_CODE => KEYPAD_CODE,
50     KEYPAD_COL => KEYPAD_COL
51 );
52
53 uKeyControl : KEY_CONTROL port map(
54     Reset => Reset,
55     Kack => Kack,
56     Kpress => KpressSignal,
57     Clk => CLK,
58     Kval => Kval,
59     Kscan => KscanSignal
60 );
61
62
63
64 end arq_KeyDecode;

```


B. Descrição VHDL do bloco *Ring Buffer*

Ring Buffer Control

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity RingBufferControl is
5  port( DAV,clk,reset, CTS, full, empty : IN STD_LOGIC;
6        Wreg, Wr, selPnG, DAC, incPut, incGet : OUT STD_LOGIC
7  );
8  end RingBufferControl;
9
10 architecture arq_RingBufferControl of RingBufferControl is
11
12  type STATE_TYPE is (WAITING, WAIT_FOR_READING, READING, ADDRESSING, WRITING, INCRPUT,
13    INCRGET, COMPLETED);
14
15  signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
16
17  begin
18    -- Registo Current State
19
20    CURRENT_STATE <= WAITING when (reset = '1') else NEXT_STATE when rising_edge(clk);
21
22    -- Mquina de Estados
23
24    GenerateNextState:
25    process (CURRENT_STATE, DAV, CTS, full, empty)
26    begin
27      case CURRENT_STATE is
28        when WAITING => if(DAV = '0' and CTS = '1' and empty = '0') then
29                          NEXT_STATE <= READING;
30                        elsif(DAV = '1' and empty = '1') then
31                          NEXT_STATE <= ADDRESSING;
32                        elsif(DAV = '1' and full = '1') then
33                          NEXT_STATE <= WAIT_FOR_READING;
34                        elsif(DAV = '1' and full = '0') then
35                          NEXT_STATE <= ADDRESSING;
36                        else
37                          NEXT_STATE <= WAITING;
38                        end if;
39
40        when ADDRESSING => NEXT_STATE <= WRITING;
41
42        when WRITING => NEXT_STATE <= INCRPUT;
43        when INCRPUT => NEXT_STATE <= COMPLETED;
44
45        when WAIT_FOR_READING=> if(CTS = '1') then
46                                NEXT_STATE <= READING;
47                              else
48                                NEXT_STATE <= WAIT_FOR_READING;
49                              end if;
50
51        when READING => if(CTS = '0') then
52                          NEXT_STATE <= INCRGET;
53                        else
54                          NEXT_STATE <= READING;
55                        end if;
56
57        when INCRGET => if(DAV = '1') then
58                          NEXT_STATE <= ADDRESSING;
59                        else
60                          NEXT_STATE <= WAITING;
61                        end if;
62
63        when COMPLETED => if(DAV = '0') then
64                              NEXT_STATE <= WAITING;
65                            else
66                              NEXT_STATE <= COMPLETED;
67                            end if;
68      end case;
69    end process;

```

```
68
69  --      Outputs
70
71
72  incGet  <= '1' when (CURRENT_STATE = INCRGET)      else '0';
73  selPnG<= '1' when (CURRENT_STATE = ADDRESSING OR CURRENT_STATE = WRITING )  else '0';
74  wreq   <= '1' when (CURRENT_STATE = READING)      else '0';
75  wr     <= '1' when (CURRENT_STATE = WRITING)      else '0';
76  incPut <= '1' when (CURRENT_STATE = INCRPUT ) else '0';
77  DAC   <= '1' when (CURRENT_STATE = COMPLETED) else '0';
78
79
80  end arq_RingBufferControl;
```

Memory Address Control

Contador de 3 bits

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Counter_3bit is
5      Port ( CLK : in  STD_LOGIC;
6            RST : in  STD_LOGIC;
7            ndecInc : in  STD_LOGIC;
8            en : in  STD_LOGIC;
9            Count : out  STD_LOGIC_VECTOR (3 downto 0));
10 end Counter_3bit;
11
12 architecture Behavioral of Counter_3bit is
13
14     COMPONENT CounterLogic_3bit
15     PORT(
16         en : IN std_logic;
17         ndecInc : IN std_logic;
18         operandA : IN std_logic_vector(3 downto 0);
19         R : OUT std_logic_vector(3 downto 0)
20     );
21     END COMPONENT;
22
23     COMPONENT register_D_R
24     GENERIC (
25         WIDTH : POSITIVE := 1
26     );
27     PORT(
28         CLK : IN std_logic;
29         RST : IN std_logic;
30         D : IN std_logic_vector(WIDTH-1 downto 0);
31         Q : OUT std_logic_vector(WIDTH-1 downto 0)
32     );
33     END COMPONENT;
34
35     signal operandA, result : std_logic_vector(3 downto 0);
36
37 begin
38
39     Inst_CounterLogic_3bit: CounterLogic_3bit PORT MAP(
40         en => en,
41         ndecInc => ndecInc,
42         operandA => operandA,
43         R => result
44     );
45
46     Inst_register_D_R: register_D_R GENERIC MAP(
47         WIDTH => 4
48     )

```

```
49     PORT MAP(  
50         CLK => CLK,  
51         RST => RST,  
52         D => result,  
53         Q => operandA  
54     );  
55  
56     Count <= operandA;  
57  
58 end Behavioral;  
59  
60
```

Contador crescente/decrescente 4 bits

```
1  library IEEE;  
2  use IEEE.STD_LOGIC_1164.ALL;  
3  
4  entity Counter_4bit is  
5      Port ( CLK : in  STD_LOGIC;  
6            RST : in  STD_LOGIC;  
7            ndecInc : in  STD_LOGIC;  
8            en : in  STD_LOGIC;  
9            Count : out  STD_LOGIC_VECTOR (3 downto 0));  
10 end Counter_4bit;  
11  
12 architecture Behavioral of Counter_4bit is  
13  
14     COMPONENT CounterLogic_4bit  
15     PORT(  
16         en : IN std_logic;  
17         ndecInc : IN std_logic;  
18         operandA : IN std_logic_vector(3 downto 0);  
19         R : OUT std_logic_vector(3 downto 0)  
20     );  
21 END COMPONENT;  
22  
23     COMPONENT register_D_R  
24     GENERIC (  
25         WIDTH : POSITIVE := 1  
26     );  
27     PORT(  
28         CLK : IN std_logic;  
29         RST : IN std_logic;  
30         D : IN std_logic_vector(WIDTH-1 downto 0);  
31         Q : OUT std_logic_vector(WIDTH-1 downto 0)  
32     );  
33 END COMPONENT;  
34
```

```

35     signal operandA, result : std_logic_vector(3 downto 0);
36
37 begin
38
39     Inst_CounterLogic_4bit: CounterLogic_4bit PORT MAP(
40         en => en,
41         ndecInc => ndecInc,
42         operandA => operandA,
43         R => result
44     );
45
46     Inst_register_D_R: register_D_R GENERIC MAP(
47         WIDTH => 4
48     )
49     PORT MAP(
50         CLK => CLK,
51         RST => RST,
52         D => result,
53         Q => operandA
54     );
55
56     Count <= operandA;
57
58 end Behavioral;
59

```

Register_D_R

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity register_D_R is
5      Generic (WIDTH : POSITIVE := 1);
6      Port (CLK : in STD_LOGIC;
7           RST : in STD_LOGIC;
8           D : in STD_LOGIC_VECTOR(WIDTH-1 downto 0);
9           Q : out STD_LOGIC_VECTOR(WIDTH-1 downto 0));
10 end register_D_R;
11
12 architecture Behavioral of register_D_R is
13
14 begin
15
16     Q <= (others => '0') when RST = '1' else D when rising_edge(clk);
17
18 end Behavioral;
19

```

Multiplexer 2x1

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity MUX2_1_3bits is
5      Port ( I0 : in  STD_LOGIC_VECTOR (2 downto 0);
6            I1 : in  STD_LOGIC_VECTOR (2 downto 0);
7            sel : in  STD_LOGIC;
8            Y : out  STD_LOGIC_VECTOR (2 downto 0));
9  end MUX2_1_3bits;
10
11 architecture Behavioral of MUX2_1_3bits is
12
13 begin
14
15     Y <= I0 when sel='0' else I1;
16
17 end Behavioral;
18
```

CounterLogic_4bit

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity CounterLogic_4bit is
5      Port ( en : in  STD_LOGIC;
6            ndecInc : in  STD_LOGIC;
7            operandA : in  STD_LOGIC_VECTOR (3 downto 0);
8            R : out  STD_LOGIC_VECTOR (3 downto 0));
9  end CounterLogic_4bit;
10
11 architecture Structural of CounterLogic_4bit is
12
13     COMPONENT adder4bit
14     PORT(
15         A : IN std_logic_vector(3 downto 0);
16         B : IN std_logic_vector(3 downto 0);
17         CI : IN std_logic;
18         R : OUT std_logic_vector(3 downto 0);
19         CO : OUT std_logic
20     );
21     END COMPONENT;
22
23     COMPONENT MUX2_1
24     PORT(
25         I0 : IN std_logic_vector(3 downto 0);
26         I1 : IN std_logic_vector(3 downto 0);
27         sel : IN std_logic;
28         Y : OUT std_logic_vector(3 downto 0)
29     );
30     END COMPONENT;
31
```

```

32     signal operandB : STD_LOGIC_VECTOR(3 downto 0) ;
33     signal increment : STD_LOGIC_VECTOR(3 downto 0) ;
34
35     begin
36
37         U2_adder4bit: adder4bit PORT MAP(
38             A => operandA,
39             B => operandB,
40             CI => '0',
41             R => R,
42             CO => open
43         );
44
45         U0_MUX2_1: MUX2_1 PORT MAP(
46             I0 => "1111",
47             I1 => "0001",
48             sel => ndecInc,
49             Y => increment
50         );
51
52         U1_MUX2_1: MUX2_1 PORT MAP(
53             I0 => "0000",
54             I1 => increment,
55             sel => en,
56             Y => operandB
57         );
58
59     end Structural;
60

```

MAC

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY MAC IS
5      PORT( MCLK,reset : IN STD_LOGIC;
6            putnget, incPut, incGet: IN STD_LOGIC;
7            full,empty : OUT STD_LOGIC;
8            Address : OUT STD_LOGIC_VECTOR(2 downto 0)
9      );
10 END MAC;
11
12
13 ARCHITECTURE arq_MAC OF MAC IS
14
15     component Counter_4bit is
16         Port ( CLK : in STD_LOGIC;
17               RST : in STD_LOGIC;
18               ndecInc : in STD_LOGIC;
19               en : in STD_LOGIC;
20               Count : out STD_LOGIC_VECTOR (3 downto 0));
21     end component;
22

```



```

23 component COUNTER_3 IS
24   PORT(
25     CLK : in std_logic;
26     E : in std_logic;
27     CLR: in std_logic;
28     R : out std_logic_vector (2 downto 0) :=(others => '0')
29   );
30
31 end component;
32
33
34 component MUX2_1_3bits is
35   Port ( I0 : in STD_LOGIC_VECTOR (2 downto 0);
36         I1 : in STD_LOGIC_VECTOR (2 downto 0);
37         sel : in STD_LOGIC;
38         Y : out STD_LOGIC_VECTOR (2 downto 0));
39 end component;
40
41
42 signal idxGetSignal, idxPutSignal : std_logic_vector(2 downto 0);
43 signal membersSignal : std_logic_vector(3 downto 0);
44 signal enableSignal : STD_LOGIC;
45
46
47 begin
48
49   enableSignal <= incPut OR incGet;
50
51   Ucounter_4 : Counter_4bit port map (
52     CLK => MCLK,
53     RST => reset,
54     ndecInc => incPut, --0 dec 1 inc
55     en => enableSignal,
56     Count => membersSignal
57   );
58
59   Ucounter_3_putIdx : COUNTER_3 port map (
60     CLK => MCLK,
61     E => incPut,
62     CLR => reset,
63     R => idxPutSignal
64   );
65
66
67   Ucounter_3_getIdx : COUNTER_3 port map(
68     CLK => MCLK,
69     E => incGet,
70     CLR => reset,
71     R => idxGetSignal
72   );
73
74
75   UMux2_1 : MUX2_1_3bits port map (
76     I0 => idxGetSignal,
77     I1 => idxPutSignal,

```

```
78         sel => putnget,  
79         Y => Address  
80     );  
81  
82     full <= membersSignal(3);  
83     empty <= not membersSignal(3) AND not membersSignal(2) AND not membersSignal(1) AND not  
84         membersSignal(0);  
85     end arq_MAC;  
86  
87  
88  
89  
90
```

C. Descrição VHDL do bloco *Output Buffer*

Output Buffer Control

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity OutputBufferControl is
5  port( clk,reset, Load, ACK : IN STD_LOGIC;
6        Wreg, OBfree, Dval : OUT STD_LOGIC
7  );
8  end OutputBufferControl;
9
10 architecture arq_OutputBufferControl of OutputBufferControl is
11
12  type STATE_TYPE is (WAITING, SENDING, COMPLETED);
13
14  signal CURRENT_STATE, NEXT_STATE : STATE_TYPE;
15
16  begin
17
18  --    Registo Current State
19
20  CURRENT_STATE <= WAITING when (reset = '1') else NEXT_STATE when rising_edge(clk);
21
22  --    Máquina de Estados
23
24  GenerateNextState:
25  process (CURRENT_STATE, Load, ACK )
26  begin
27      case CURRENT_STATE is
28          when WAITING => if(Load = '1') then
29                          NEXT_STATE      <= SENDING;
30                      else
31                          NEXT_STATE      <= WAITING;
32                      end if;
33
34          when SENDING =>    NEXT_STATE      <= COMPLETED;
35
36          when COMPLETED => if(ACK = '1') then
37                              NEXT_STATE      <= WAITING;
38                          else
39                              NEXT_STATE      <= COMPLETED;
40                          end if;
41
42          end case;
43  end process;
44
45  --    Outputs
46
47
48  OBfree <= '1' when (CURRENT_STATE = WAITING)      else '0';
49  Dval <= '1' when (CURRENT_STATE = COMPLETED)      else '0';
50  Wreg <= '1' when (CURRENT_STATE = SENDING)      else '0';
51
52
53
54  end arq_OutputBufferControl;

```

Registor

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY REGISTOR IS
5      PORT( R : in std_logic_vector(3 downto 0);
6            CLR : in std_logic;
7            CL : in std_logic;
8            E : in std_logic;
9            TC : out std_logic;
10           F : out std_logic_vector (3 downto 0)
11         );
12  END REGISTOR;
13
14
15  ARCHITECTURE arq_REGISTOR OF REGISTOR IS
16
17  COMPONENT FFD
18      PORT( CLK : in std_logic;
19            RESET : in STD_LOGIC;
20            SET : in std_logic;
21            D : IN STD_LOGIC;
22            EN : IN STD_LOGIC;
23            Q : out std_logic
24          );
25  END COMPONENT;
26
27  SIGNAL Res: std_logic_vector(3 downto 0);
28
29
30  BEGIN
31
32  F <= Res;
33
34  TC <= not Res(0) and not Res(1) and not Res(2) and not Res(3);
35
36  U0FFD : FFD port map(
37      CLK => CL,
38      RESET => CLR,
39      SET => '0',
40      D => R(0),
41      EN => E,
42      Q => Res(0)
43  );
44
45  U1FFD : FFD port map(
46      CLK => CL,
47      RESET => CLR,
48      SET => '0',
49      D => R(1),
50      EN => E,
51      Q => Res(1)
52  );
53
54  U2FFD : FFD port map(
55      CLK => CL,
56      RESET => CLR,
57      SET => '0',

```

```

58     D => R(2),
59     EN => E,
60     Q => Res(2)
61 );
62
63 U3FFD : FFD port map(
64     CLK => CL,
65     RESET => CLR,
66     SET => '0',
67     D => R(3),
68     EN => E,
69     Q => Res(3)
70 );
71
72 END arq_REGISTER;

```

Output Buffer

```

1  LIBRARY IEEE;
2  USE IEEE.std_logic_1164.all;
3
4  ENTITY Output_Buffer IS
5      PORT( MCLK,reset : IN STD_LOGIC;
6            Load, ACK: IN STD_LOGIC;
7            Dval, OBfree : OUT STD_LOGIC;
8            Din : IN STD_LOGIC_VECTOR(3 downto 0);
9            Q : OUT STD_LOGIC_VECTOR(3 downto 0)
10     );
11  END Output_Buffer;
12
13
14  ARCHITECTURE arq_Output_Buffer OF Output_Buffer IS
15
16
17
18  COMPONENT OutputBufferControl is
19  port( clk,reset, Load, ACK : IN STD_LOGIC;
20        Wreg, OBfree, Dval : OUT STD_LOGIC
21  );
22  END COMPONENT;
23
24
25  COMPONENT REGISTER IS
26  PORT( R : in std_logic_vector(3 downto 0);
27        CLR : in std_logic;
28        CL : in std_logic;
29        E : in std_logic;
30        TC : out std_logic;
31        F : out std_logic_vector (3 downto 0)
32  );
33  END COMPONENT;
34
35  signal WregSignal :STD_LOGIC;
36
37  begin
38

```

```
--
39  UOutputBufferControl : OutputBufferControl port map(
40      clk      => MCLK,
41      reset    => reset,
42      Load    => Load,
43      ACK      => ACK,
44      Wreg     => WregSignal,
45      OBfree   => OBfree,
46      Dval     => Dval
47  );
48
49  UREGISTOR : REGISTOR port map(
50      R      => Din,
51      CLR    => reset,
52      CL     => MCLK,
53      E      => WregSignal,
54      F      => Q
55  );
56
57  end arq_Output_Buffer;
```

Keyboard Reader

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Keyboard_Reader is
5  port( CLK, Reset, ACK : IN STD_LOGIC;
6        Dval : OUT STD_LOGIC;
7        KEYPAD_LIN : in std_logic_vector(3 downto 0);
8        KEYPAD_COL : out std_logic_vector(3 downto 0);
9        Q : out std_logic_vector(3 downto 0)
10 );
11 end Keyboard_Reader;
12
13 architecture arq_Keyboard_Reader of Keyboard_Reader is
14
15
16
17 component Ring_Buffer IS
18   PORT( MCLK,reset : IN STD_LOGIC;
19         DAV, CTS: IN STD_LOGIC;
20         DAC, Wreg : OUT STD_LOGIC;
21         Din : IN STD_LOGIC_VECTOR(3 downto 0);
22         Q : OUT STD_LOGIC_VECTOR(3 downto 0)
23   );
24 end component;
25
26
27 component Output_Buffer IS
28   PORT( MCLK,reset : IN STD_LOGIC;
29         Load, ACK: IN STD_LOGIC;
30         Dval, OBFfree : OUT STD_LOGIC;
31         Din : IN STD_LOGIC_VECTOR(3 downto 0);
32         Q : OUT STD_LOGIC_VECTOR(3 downto 0)
33   );
34 end component;
35
36 component Key_Decode is
37 port( Kack,CLK,Reset : IN STD_LOGIC;
38       Kval : OUT STD_LOGIC;
39       KEYPAD_LIN : in std_logic_vector(3 downto 0);
40       KEYPAD_CODE: out std_logic_vector(3 downto 0);
41       KEYPAD_COL : out std_logic_vector(3 downto 0)
42 );
43 end component;
44
45
46
47 --component CLKDIV is
48 --generic(div: natural := 50000000);
49 --port ( clk_in: in std_logic;
50       -- clk_out: out std_logic);
51 --end component;
52
53
54 signal WregSignal, Clk_signal, OBFfreeSignal,DAVSignal , DACSignal : STD_LOGIC;
55 signal codeSignal,QSignal : STD_LOGIC_VECTOR(3 downto 0);
56
57 begin
58
59
60 --uCLKDIV : CLKDIV generic map(2) port map(
61   -- clk_in => CLK,
62   --clk_out => Clk_signal
63 --);
64

```



```

78         MCLK => CLK,
79         reset => reset,
80         Load => WregSignal,
81         ACK => ACK,
82         Dval => Dval,
83         OBfree => OBfreeSignal,
84         Din => QSignal,
85         Q => Q
86     );
87
88     uKey_Decode : Key_Decode port map(
89         Reset => reset,
90         CLK => CLK,
91         Kack => DACSignal,
92         Kval => DAVSignal,
93         KEYPAD_LIN => KEYPAD_LIN,
94         KEYPAD_CODE => codeSignal,
95         KEYPAD_COL => KEYPAD_COL
96     );
97
98     uRing_Buffer : Ring_Buffer port map(
99         MCLK => CLK,
100        reset => reset,
101        DAV => DAVSignal,
102        CTS => OBfreeSignal,
103        DAC => DACSignal,
104        Wreg => WregSignal,
105        Din => codeSignal,
106        Q => QSignal
107    );
108
109    uOutput_Buffer : Output_Buffer port map(

```

D. Descrição VHDL do bloco KeyboardReaderUSBPORT

```

1  library IEEE;
2  use IEEE.std_logic_1164.all;
3
4  entity Keyboard_ReaderUSBPORT is
5  port( CLK, Reset : IN STD_LOGIC;
6        KEYPAD_LIN : in std_logic_vector(3 downto 0);
7        KEYPAD_COL : out std_logic_vector(3 downto 0)
8
9  ) ;
10 end Keyboard_ReaderUSBPORT;
11
12 architecture arq_Keyboard_Reader of Keyboard_ReaderUSBPORT is
13
14  COMPONENT UsbPort IS
15      PORT
16      (
17          inputPort: IN STD_LOGIC_VECTOR(7 DOWNTO 0);
18          outputPort : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
19      );
20  END COMPONENT;
21
22
23  component Keyboard_Reader is
24  port( CLK, Reset, ACK : IN STD_LOGIC;
25        Dval : OUT STD_LOGIC;
26        KEYPAD_LIN : in std_logic_vector(3 downto 0);
27        KEYPAD_COL : out std_logic_vector(3 downto 0);
28        Q : out std_logic_vector(3 downto 0)
29
30  );
31  end component;
32
33
34  signal WregSignal, Clk_signal, OBfreeSignal,DAVSignal , DACSignal : STD_LOGIC;
35  signal codeSignal,QSignal : STD_LOGIC_VECTOR(3 downto 0);
36  signal UsbPortInputSignal, UsbPortOutputSignal : STD_LOGIC_VECTOR (7 downto 0);
37
38  begin
39
40
41  uUsbPort: UsbPort PORT MAP(
42      inputPort => UsbPortInputSignal,
43      outputPort => UsbPortOutputSignal
44  );
45
46
47  uKeyboardReader : Keyboard_Reader port map(
48      CLK => CLK,
49      Reset => reset,
50      ACK => UsbPortOutputSignal(7), --ver no KBD
51      Dval => UsbPortInputSignal(4), --ver no KBD
52      KEYPAD_LIN => KEYPAD_LIN,
53      KEYPAD_COL => KEYPAD_COL,
54      Q => UsbPortInputSignal(3 downto 0) --ver no KBD
55  );
56
57
58
59  end arq_Keyboard_Reader;

```

E. Atribuio de pinos do mdulo *Keyboard_ReaderUSBPORT*

```
#=====
# CLOCK
#=====

set_location_assignment PIN_P11 -to CLK
#=====
#SWITCHES
#=====
set_location_assignment PIN_C10 -to Reset

#=====

set_location_assignment PIN_W5 -to KEYPAD_LIN[0]
set_location_assignment PIN_AA14 -to KEYPAD_LIN[1]
set_location_assignment PIN_W12 -to KEYPAD_LIN[2]
set_location_assignment PIN_AB12 -to KEYPAD_LIN[3]
set_location_assignment PIN_AB11 -to KEYPAD_COL[0]
set_location_assignment PIN_AB10 -to KEYPAD_COL[1]
set_location_assignment PIN_AA9 -to KEYPAD_COL[2]
set_location_assignment PIN_AA8 -to KEYPAD_COL[3]
#=====
# End of pin and io_standard assignments
#=====
```

F. Código Kotlin - HAL

```
object HAL {
    var written = 0b0000_0000
    private var ACTIVE = false
    fun init() { // Inicia a classe
        if(!ACTIVE) {
            UsbPort.write(written)
            ACTIVE=true
        }
    }
}

// Retorna true se o bit tiver o valor lógico '1'
fun isBit(mask: Int): Boolean = (mask and UsbPort.read()) != 0

// Retorna os valores dos bits representados por mask presentes no UsbPort
fun readBits(mask: Int): Int = mask and UsbPort.read()

// Escreve nos bits representados por mask o valor de value
/**
 * value -> 0000_1001.
 * mask -> 0000_1111.
 * lastWritten -> 1111_0111.
 * new lastWritten -> 1111_1001.
 * 1º: (value and mask) -> 0000_1001 sets the bits in value to be written to the ones in the
mask.
 * 2º: (lastWritten and mask.inv()) -> 1111_0000 sets the bits in lastWritten that are not
in the mask,this operation
 *     sets to 0 all the bits in lastWritten that are not in the mask, preparing it to
receive the updated value.
 * 3º: (value and mask) or (lastWritten and mask.inv()) -> 0000_1001 or 1111_0000 ->
1111_1001 sets the bits in
 *     lastWritten that are in the mask to the corresponding bits in value and keeps the
bits that are not in the mask unchanged.
 */

fun writeBits(mask: Int, value: Int) {
    written = (value and mask) or (written and mask.inv())
    UsbPort.write(written)
}

// Coloca os bits representados por mask no valor lógico '1'
fun setBits(mask: Int) {
    written = (written or mask)
    UsbPort.write(written)
}

// Coloca os bits representados por mask no valor lógico '0'
fun clrBits(mask: Int) {
    written = written and mask.inv()
    UsbPort.write(written)
}
}
```

G. Código Kotlin - KBD

```
//
/**
 * Mapeamento das teclas do teclado matricial 4x4:
 *
 *      Key   Column 1   Key Column 2   Key Column 3
 * *Row 1    1    0x00    2    0x04    3    0x08
 * *Row 2    4    0x01    5    0x05    6    0x09
 * *Row 3    7    0x02    8    0x06    9    0x0A
 * *Row 4    *    0x03    0    0x07    #    0x0B
 */

//Read keys. Methods return '0'..'9','#','*' or NONE.
object KBD {
    const val NONE = 0.toChar()
    const val DATA = 0x0F //UsbPort.IO..3
    const val MASK_DVAL = 0x10 //UsbPort.I4
    const val MASK_ACK = 0x80 //UsbPort.O7
    private val KEYS : List<Char> = listOf('1', '4', '7', '*', '2', '5', '8', '0', '3', '6', '9',
    '#')
    // 0 1 2 3 4 5 6 7 8 9 10
11
    // Starts the class.
    fun init() {
        HAL.init()
    }
    // Returns the pressed or NONE key immediately if there is no key pressed.
    fun getKey(): Char {
        if (HAL.isBit(MASK_DVAL)) {
            val a = HAL.readBits(DATA)
            return if (a in 0..11) {
                HAL.setBits(MASK_ACK)
                HAL.clrBits(MASK_ACK)
                KEYS[a]
            } else NONE
        }
        return NONE
    }
    // Returns when the key is pressed or NONE after millisecond timeout has elapsed.
    fun waitKey(timeout: Long): Char {
        var time = timeout
        while (time > 0) {
            val serial = getKey()
            if (serial != NONE) return serial
            Thread.sleep(1)
            time--
        }
        return NONE
    }
}
```